

Secure Voice Signal Processing

SVSP

SafeTalk

8-bit Secure Signal Processing
Final Report

Jodie Au
Josh Chong
Tam Paredes
Jeff Sieben
Amelia Yeoh

Declaration of Original Content

The project and the contents of this report are entirely the original work of the authors except as follows:

Figures

Figure 2.2.1 taken from reference [3]
Figure 2.2.2 taken from reference [3]
Figure 2.2.3 taken from reference [3]
Figure 2.3.1 taken from reference [5]
Figure 2.3.2 taken from reference [5]
Figure 2.3.3 taken from reference [5]
Table 2.3.1 taken from reference [5]

VHDL Files

clock_divider.vhd taken from reference [7]
input_reader.vhd modified from reference [7]
fifo.vhd taken from reference [6]
txmit.vhd modified from reference [5]
rxcvr.vhd modified from reference [5]

Jodie Au: _____

Josh Chong: _____

Tam Paredes: _____

Jeff Sieben: _____

Amelia Yeoh: _____

Table of Contents

1. Achievements	1
1.1 ADC.....	2
1.2 Encryption/Decryption.....	2
1.3 Transmitter/Receive.....	3
1.4 DAC.....	3
1.5 Compression/Decompression.....	3
2. Operation	4
2.1 ADC.....	4
2.2 Compression/Decompression.....	14
2.3 Encryption/Decryption.....	15
2.4 Transmitter/Receive.....	19
2.5 DAC.....	23
3.I/O Signals	26
4. Design Hierarchy.....	32
5. FPGA Resources	34
5.1 ADC.....	34
5.2 Encryption/Decryption.....	34
5.3 Transmitter/Receive.....	34
6. Experimentation	40
6.1 Transmitter/Receive.....	35
6.2 Compression/Decompression.....	35
7. Integrated Test Measurements (Not Included).....	37
8. Research.....	37
9. References.....	39
10. Test Case Index	40
12. VHDL Source Code Index.....	63
13. Test Bench Index.....	64
A. Appendix : Data Sheets	65

1. Achievements

The SafeTalk prototype has been very successful in design, simulation, and implementation. The experimentation is promising and the outlook for future versions of SafeTalk is positive. The speech signal has been successfully converted to a digital signal and back into an analog signal. This milestone set the tone for successes during the remainder of the project. The transmission and receiving modules of SafeTalk were the cornerstones in the final result. A universal asynchronous receive transmitter (UART) simulated properly, and because it was asynchronous it transmitted and received encrypted data automatically. As well, the simulations correctly indicate that the framing and parity error checking mechanism was in place. Finally, the encryption module is designed to allow for a stronger algorithm to secure speech data. The most exciting part of the encryption module is that the data is not audibly recognizable if converted to analog. Even though the cipher that was used is not secure by some standards, your roommate could not tell what you were saying to your friends on the other line.

The entire design of SafeTalk comprises of many different subsections. A lot of our objectives and goals were achieved although we must admit that there are still a number of small sub-sections that has

The achievements obtained throughout the entire duration of our project is briefly explained in the table below:

	COMPILATION SUCCESSFUL	SIMULATION WAVEFORM AS EXPECTED	CODE IMPLEMENTATION WITH HARDWARE &/OR FPGA BOARD WITH CORRECT OUTPUTS
ADC hardware	√	√	√
DAC hardware	√	√	√
ADC & DAC	√	√	√
Compression	x	x	x
Encryption Code (EC)	√	√	√
Encryption with ADC	√	√	√
Encryption with Transmission	√	√	√
Decryption Code (DC)	√	√	√
Decryption with DAC	√	√	√
Decryption with Receiver	√	√	√
Transmission Code (TC)	√	√	√
Receiver Code (RC)	√	√	~
TC & RC with controller	√	√	~
TC, RC, controller with FIFO buffer	√	√	~
TC & RC with ADC & DAC hardware	√		~
ADC hardware, EC, & TC	√	√	√
DAC hardware, DC, & RC	√	x	√

1.1 ADC

The ADC design has hardware and software components. The hardware component consists of an analog circuit with 2 operational-amplifiers, one low pass filter, one Sample & Hold chip, and an ADC0809 chip. This circuit performs correctly when connected to the FLEX10K board using the function generator / microphone to generate an input signal.

The waveforms observed on the oscilloscope are as expected. Output signals are verified to be similar to that of the input signal. Signals like *sample*, *SOC*, *EOC*, and *clock* (of the ADC0809) were also probed on the oscilloscope to verify correctness. These again match the expected values. The simulation waveforms for the various test cases are enclosed in this document.

The software component consists of two VHDL programs – *input_reader.vhd* & *clock_divider.vhd*. Both VHDL programs simulated correctly without any glitches. Refer to the simulation waveforms enclosed in this document.

Attempts were also made to connect the ADC with the DAC. The function generator was used as an input, because the signal it produces is much more consistent a human voice input. The output produced by the DAC circuits are exactly identical to that of the input waveform produced by the function generator except for a slight delay and amplification in the output signal, thus confirming the fact that the analog-digital-analog conversion process works. Although there were some noise interference in the output waveform, the voices transmitted were relatively audible. The input waveforms used for testing varied from a sinusoidal wave to a square wave to a triangular waveform, which gave a range of different inputs to test. The outputs are identical to that of the input. The clock frequency used for testing purposes was approximately 840kHz (divisor value for *clock_divider.vhd* is 15). When a microphone was used as an input, voices can be heard through the speaker. Although there was some noise interference, the sound quality was quite satisfactory. The ADC module functions correctly.

1.2 Encryption/Decryption

The stream cipher operates correctly in both the encryption and decryption stages. Tests were performed on the FPGA to ensure its correct operation. The parallel-to-serial and serial-to-parallel converters were also successfully interfaced with the input and output, respectively, of the stream cipher. Furthermore, the encryption VHDL entity was successfully connected to the ADC entity. The tests performed with the ADC hardware and the FPGA show promising results. The outputs of the encryptor are non-periodic square waves that correspond to the binary logic 0's and 1's that are the expected outputs of the encryptor. The decryption VHDL entity was also successfully integrated with the DAC hardware. The tests performed show that this compound entity properly decrypts data.

However, the attempts to integrate these compound entities (i.e. ADC/encryptor and decryptor/DAC) with the transmitter and receiver, respectively, have not been successful. As well, integration of the compound entities with the DSP controller is not currently successful.

It must be noted that the stream cipher in this project is based on linear shift registers. This type of implementation for the stream cipher is not considered strong security. The

reason for choosing this implementation is that it is simpler than most other stream ciphers or block ciphers. So it is fast to implement and is more realistic for the scope of our project. It allowed us to complete the encryption/decryption stages and to test it with the rest of the system. The limitations of this cipher are noted, and as such, the cipher entity was built as a completely separate module, so it can more easily be replaced by a more complex and more secure cipher if time permitted. The success of completing this simple cipher used can be regarded as a successful step in fully implementing SafeTalk

1.3 Transmitter/Receive

The UART is used in the transmission of the digital data, which is obtained from the DAC and encrypted in the FPGA. The original files obtained from QuickLogic partially worked. With some experimentation and testing both the transmitter and receiver modules were modified to transmit and receive properly in the simulations. The problem arises when the code is uploaded to the FPGA and executed. For reasons that are not determined the correct reception of data did not occur correctly in spite of the results obtained from the simulations. Framing errors and parity errors occurred frequently. In the end we were able to get the UART to transmit and receive without errors. The proper transmission/reception of the data was achieved after careful testing. The modifications were made to allow the proper transmission.

1.4 DAC

All of tests performed by the DAC shows that the DAC works successfully. The DAC accepts an 8-bit digital data and converts it to an analog signal. Using three test cases, we are able to conclude that the DAC works as expected. Using either the manual switches from the UP1 board or a counter written in VHDL code as the input, the DAC successfully converts both digital signals to analog waveforms.

Finally, testing the DAC with the ADC verifies the all conclusions made for the DAC. The output signal is identical to the input signal (microphone/function generator) except for some propagation delay and signal amplification. The design and use of the DAC is verified as a completed step towards the success of SafeTalk.

1.5 Compression/Decompression

When a speech signal is compressed the redundancies in information are removed because they are not needed to reconstruct the signal. That way only relevant information is utilized. The conversion of an audio signal from analog to digital is simple, however, the data that results in the conversion to digital is large compared to the data needed to reconstruct it and convert it back to analog. As a result a large speed modem—64Kbps—would be required to send all the information. This modem speed can not be obtained with the resources available therefore compression is needed.

The members did not have any basis as to how compression worked, and therefore research started at the search engines on the Internet. The outcome of the research is that knowledge is gained in the areas of speech characteristics and speech compression. The compression algorithm is an amateur design that reduces the number of bits to represent the digital speech signal. Samples are converted at 840KHz, so to keep the massive amounts of data passing through to the UART, 1 in every 8 samples is removed. This provides an effective sample of 8KHz. The design and simulation of the compression is documented in this document.

2. Operation

2.1 ADC

The analog-to-digital converter is broken up into the hardware design and the software design.

For the hardware design, the circuit is divided into 5 sub-sections:

1. Audio Condenser Microphone (AM 242)
2. Analog Operational Amplifiers (LM324)
3. Low Pass Filter (LF351)
4. Sample and Hold (SMP11)
5. A/D converter (ADC0809)

2.1.1

SafeTalk uses a condenser microphone with an internal resistance of approximately 2k . It is a NCAT (Noise Canceling and Amplification Technology) microphone for accurate voice input. According to the specification sheet, the sensitivity of the microphone is – 67dB/uBar, -47dBV/Pascal \pm 4dB. The frequency response of the microphone ranges from 100-16,000Hz.

2.1.2

The microphone signal amplification is done in two stages with a pre-amplifier and an actual amplifier. The breakdown of this sub-section into the two amplifiers is done in order to avoid oscillations and non-ideal operations of the op-amp at very high gain configurations. Both amplifier stages are built using an LM324 (**Figures 2.1.1, 2.1.2**) single-ended op-amp. The LM324 series DIP consists of four independent, high-gain, internally frequency compensated operational amplifiers that are designed specifically to operate from a single power over a wide range of voltages. For our design, a single power supply set at 5V DC is used to drive the amplifier system. Note that doing this does indeed limit the positive output to 4.2V, this limitation can be rectified in the A/D section.

 


Figure 2.1.1: Pre-Amplifier Schematic

The pre-amplification (**Figure 2.1.1**) stage provides the main source of gain for the amplifier. The op-amp configuration used here is an inverting single-ended amplifier. The reason the chip is connected to a $\pm 12V$ power supply instead of a $+5V$ and ground signal is to account for the clipping that occurred in the outputs of the amplifier. Both the capacitors used here are of values $10\mu F$ and they provide DC blocking and a signal ground. The gain for this amplifier is given by the formula $(110k/250) = 440$. Note that the gain value here is theoretical and practical results may differ.

2.1.3

 


Figure 2.1.2: Amplifier Schematic

The design for the main amplifier stage (**Figure 2.1.2**) is very similar to that of the pre-amplifier stage. However, the only difference is that the 250Ω resistor is replaced with a 1-10kΩ potentiometer that provides the user with the flexibility to adjust the microphone sensitivity. The reason we are using +12V and -12V for the power supplies of the chip instead of +5V and ground in order to achieve a higher voltage range and to avoid clipping in the waveforms.

2.1.4

 


Figure 2.1.3: Low Pass Filter Schematic

A low pass filter design is added to the ADC design to reduce noise interference. A low pass filter allows all frequencies below a certain point, known as the cutoff frequency, to pass without attenuation while suppressing all frequencies above the cutoff. The cutoff frequency is determined by the values of the capacitors C1 and C2 and resistor R1 and R2. C1 and C2 are equal in value, as are R1 and R2. The cutoff frequency is determined by the following formula:

$$\text{Cutoff} = \frac{1}{2\pi RC}$$

The cutoff frequency we are using is 4kHz (since typical bandwidth of voice signals is approximately 3kHz). Therefore, rearranging the formula above gives

$$R_4 = \frac{1}{(\text{cutoff})(C)(2\pi)} = \frac{1}{(4\text{kHz})(10\mu\text{F})(2\pi)} = 3.98\text{k}\Omega$$

The gain of this filter is equal to R4 divided by R3. The gain for this filter is 3.9kΩ/ 39Ω = 100 where R4 = 3.9 kΩ and R3 = 39Ω. R1 = R2 = 39Ω. The output at the cutoff frequency is equal to 0.707 of this circuit's maximum output.

Table 2.1.1: LF 351 Pin Connections

Pin Number on LF351	Signal Name	Connected to	Reason
4	V+	+12V (Active High)	In order for chip to function efficiently
7	V-	-12V	In order for chip to function efficiently
2	Input-	Input of filter	Transmit data
3	Input+	Input for filter	Transmit data
6	Output	SMP11 chip input (Pin 2- SMP11)	In order to transmit the appropriate signals for functionality

2.1.5

 


Figure 2.1.4: Sample and Hold Block Schematic

The sample and hold chip (SMP11) samples rapidly changing inputs (voice waveform) in order to provide a stable value for the A/D converter over a period of time. See **Figure 2.1.4** for the schematic circuit.

The sample and hold (S&H) chip provides the A/D converter with a stable value over a certain period of time in order for the A/D chip to perform the conversion efficiently. The need for the S&H chip is essential in order to provide the A/D chip with a constant value instead of a rapidly changing input—such as the waveform generated from human voices.

From the specification sheets, the sample time takes about 1.5us and the hold time is approximately 100us. It is important to note that the S&H chip requires at least 12V to operate efficiently although this is not explicitly stated in the specification sheet of the chip. For the value of *Chold*, the typical value of 0.005uF is used. This allows for a sample time of 0.75us (90% input) on a signal and a maximum of 5V swing. To allow imperfections of the chip or the circuit, the S&H time is chosen to be 1.5us.

The maximum voltage for the A/D chip is $V_{cc} + 0.3V$. Since the S&H chip can output 12 volts at full swing, two protection diodes are added onto the output of the S&H chip as shown in the figure above to clamp the output between $V_{cc} + V_{diode}$ and $Gnd - V_{diode}$.

The S&H chip requires that the signal be low for hold and high for sample. The duration of time when the signal is low (hold=100us) is much longer than the duration of time when signal is high (sample=1.5us). Control of it is done through the VHDL code entitled *input_reader.vhd*.

Some important connections for the SMP11 chip are shown in **Table 2.1.2**.

Table 2.1.2: SMP11 Pin Connections

Pin Number on SMP11	Signal Name	Connected to	Reason
9	V+	5V (Active High)	In order for chip to function efficiently
5	V-	Ground	In order for chip to function efficiently
2	Input	Output of filter (Pin 6 – LF351)	Transmit data
7	Output	Input, IN0 for ADC0809	Transmit data
14	Sample	FLEX10K board	In order to receive the appropriate signals for functionality
11	Hold Capacitor	0.005uF capacitor	Chip Requirement

2.1.6

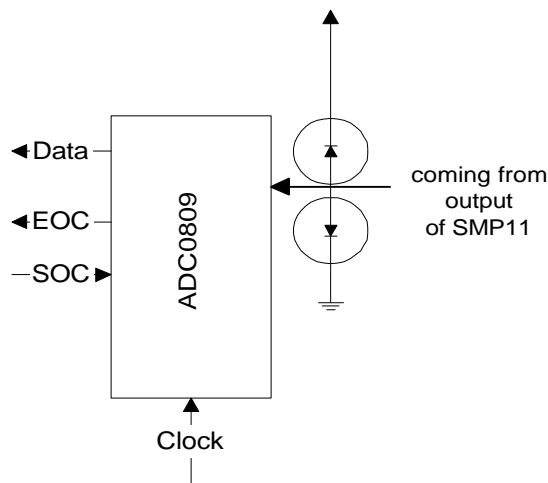


Figure 2.1.5: A/D Converter

For the A/D conversion, we use the data acquisition component (ADC0809) with an 8 bit analog-to-digital converter and an 8-channel multiplexer. The 8-bit converter uses successive approximation as the conversion technique. The advantage of this chip is that the 8-channel multiplexer can access any of 8-single-ended analog signals. However, for our design purposes, we are only using one analog channel input, IN0. The input/outputs of the chip are as in **Table 2.1.3**.

Some important facts about the ADC809 signals to familiarize with before implementation:

CLOCK:

According to the specification sheets for this chip, the input clock can be within the range of 10kHz to 1280 kHz with the typical frequency of 640kHz. For our design, we have set the input clock frequency to be approximately 840kHz thus giving us the divisor value (*clock_divider.vhd*) of approximately $(25.175\text{MHz} / (2 * 840\text{kHz})) = 15$. This frequency value is chosen so that it may be compatible with the clock frequency of that of the digital-to-analog converter.

Note that the clock entering the ADC0809 is actually the *slow_clock* generated from the program *clock_divider.vhd* and it is not the actual (central) clock. The reason the *slow_clock* is used instead of the main clock generated by the main control (FPGA), is to enable the ADC0809 and the SMP11 chips to function efficiently (chip limitations). The *slow_clock* signal generated by *clock_divider.vhd* is a factor of $(2 * \text{divisor})$ slower than the main clock. The *slow_clock* is also falling-edge triggered as oppose to that of the main clock that is rising edge triggered.

SOC:

With the SOC signal, the duration of time when the signal is high is shorter than that when the signal is low (conversion process takes approximately 100us). The signal stays high for one *slow_clock* cycle. The conversion of the analog signal to a digital signal begins as soon as the SOC signal drops to a zero from a one.

EOC:

At the end of conversion (EOC) the EOC signal goes to a zero. When the conversion process is taking place, the EOC signal remains at a one. The state machine remains at state2 (in_conv) as long as the EOC signal is high. Note also that the outputs of the data register are updated one clock cycle before the rising edge of the EOC.

CONVERSION TIME:

It takes 100us for the chip to convert a signal from analog to digital for a 840kHz frequency clock.

Some important connections for the ADC0809 chip are as follows:

Table 2.1.3: ADC0809 Pin Connections

Pin Number on ADC0809	Signal Name	Connected to	Reason
11	V _{CC}	5V (Active High)	In order for chip to function efficiently
12	V _{REF(+)}	5V (Active High)	In order for chip to function efficiently
16	V _{REF(-)}	Ground	In order for chip to function efficiently
13	Gnd	Ground	In order for chip to function efficiently
26	IN0	Analog Input (Microphone / Function Generator)	
6	SOC	FLEX10K Board	Programming Needs
7	EOC	FLEX10K Board	Programming Needs
10	Clock	FLEX10K Board	To connect to slow_clock generated by clock_divider.vhd
9	Output Enable	5V (Active High)	Outputs fed directly into the FPGA and not used in the bus configuration
25, 24, 23	Address Lines	000	IN0 is used as the input channel
22	Address Latch Enable	5V (Active High)	The select lines do not vary

 


Figure 2.1.6: Schematic of Complete ADC

The software section of this A/D basically consists of 2 VHDL programs:

1. *clock_divider.vhd*
2. *input_reader.vhd*

The purpose of *clock_divider.vhd* is to decrease the speed of the central clock by a factor of (2 * divisor). The inputs for this program are the main *clock* and *reset*. The output consists of the *slow_clock* signal. The *slow_clock* signal is generated by the clock and provides the ADC0809 and the SMP11 chips with the appropriate clock timing to function efficiently.

The *input_reader.vhd* is program consists of a finite state machine that controls the performance of the A/D chip. The design of the state machine is implemented in the following states. See **Figure 2.1.7** for the state machine.

At the first state, *sample_conv*, the data is taken in and sampled for 1.5us and held for 100us. During sampling, the signal will be high and at hold, the sample signal will drop to low.

At *start_conv*, the whole conversion process begins. *Sample* is set to zero to hold the data while the *SOC* signal is set to one; the chip must hold the data in a stable value before conversion starts. Note that conversion starts at the falling edge of the *SOC* signal. The *SOC* signal remains at one only for one complete period of *slow_clock* and when the signal drops to zero, that is when the conversion process will start. Recall the *slow_clock* is falling-edge triggered, therefore when the *slow_clock* signal goes high, the *SOC* signal goes high. When *SOC* goes to the value of zero, the *SOC* signal drops back to zero as well.

At *in_conv*, the conversion is taking place. *SOC* signal is set back to one. Recall again the *EOC* signal transitions to 1 when the conversion ends. If *EOC* is zero, *state* remains in state *in_conv*. Otherwise, *state* proceeds on to *end_conv* state.

At the next falling edge of the *slow_clock*, the state proceeds from *end_conv* to *read_conv*. Here *bits* is assigned to the dummy variable, *hold_out* and *sample* is set back to one. Finally, at the next falling edge of *slow_clock*, *state* goes back to *sample_conv*..

Now, the entire cycle repeats itself.

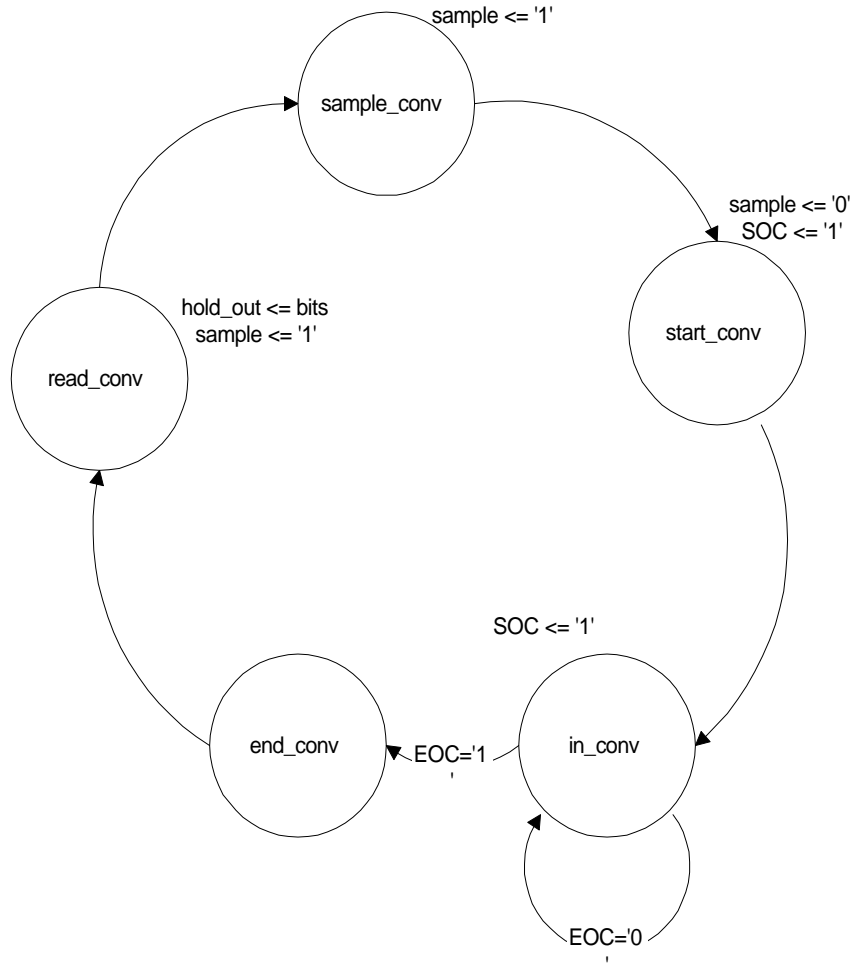


Figure 2.1.7: FSM Transition Diagram for input_reader.vhd

2.2 Compression/Decompression

The method used to compress the digital signal removes selected samples from the original signal. The basis of the compression scheme is the Nyquist Theorem that states a signal can be successfully recreated if 2 samples per period are taken. The sampling rate of the ADC is about 840KHz, and for the purpose of this project this rate is too high. Please refer to the ADC details for why 840KHz was chosen. The sample rate that Nyquist suggests is around 6-8KHz which means that several hundred thousand samples will be removed.

The way that the compressor works is the digital input is received and down sampled for the benefit of data transfer. As mentioned in earlier documents an (8 KHz sample rate) X (8 bits per sample) is 64000 Bits per second. This is impossible over the phone line, so we need to reduce this somehow. The actual sample rate is somewhere around 840KHz so every 840,000 samples one 8-bit sample is allowed to pass through. This is fine for the quality of the signal at the output of this application because we are not aiming for quality we are aiming for security. With this in mind the compressor can simply remove $840\text{KHz} - 4\text{KHz} = 836\text{KHz}$ sample from the signal.

The enable input must be high for the compressor to start doing anything. Once this is high the compressor begins to check for valid data. If the controller lets the compressor know that there is a problem with the data then this is another sign that the compressor will stop working.


The last two flags are directly related to the valid out signal in that if either of these 2 signals are clear (low) then the compressor will allow the valid out signal to be low as well. This is to prevent the controller from getting ahead of itself and encrypting data that is not available.

The main controller controls the active high enable input. This controls whether the compressor is on or not. The valid_in flag is an input that comes from the controller to tell the compressor if the data is good or not. If the data is good then the compressor compresses, and vice versa. Valid in is active high. The valid_out flag is an output that the compression stage sets. When a problem occurs — i.e. if the input is not valid — then valid_out flag is set. Valid out is active high. The input signal is an 8-bit vector that comes in from the ADC. When enable is high and the data is good the 8 bits are allowed into the compression stage and compression takes place. The output of the compression stage is an 8-bit vector as well. This vector holds the sample that is sent to the encryption stage.

The decompressor works just the opposite of the compressor. The signal arrives from the decryption stage and then it is held in a register for a about 836KHz of the input/ADC clock cycle. Much like the ADC, the decompressor takes a sample and holds it until the next sample arrives at its input.

The decompression component has the same IO as the compression component although it is implemented for decompression. The main controller controls the active high enable input. Like the compression this tells the decompressor whether or not to decompress. The valid in flag is an input that the main controller uses to let the decompressor know that decompression should be done. The valid out flag is set or cleared by the decompressor when data is not good. The input signal is an 8-bit digitized-decompressed audio signal that comes from the decryption stage of the application. The output signal is also an 8-bit decompressed signal that is passed onto the DAC for conversion back to audio.

Figure 2.2.1: Compressor/Decompressor Block Diagram

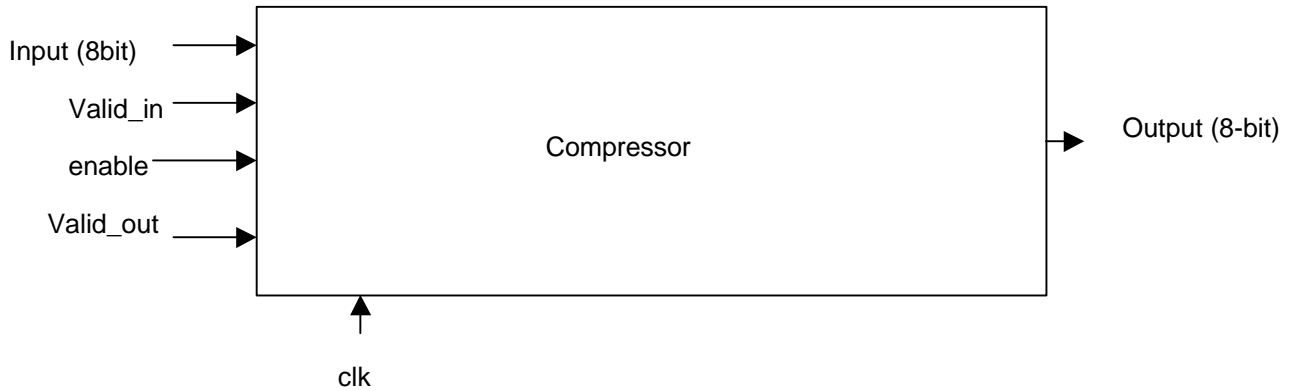

2.3 Encryption/Decryption

For the encryption stage, a stream cipher is used since stream ciphers are more suitable for hardware implementation and real-time systems where bits of data are received serially—as in the case of SafeTalk.

Stream ciphers convert plaintext to ciphertext one bit at a time. The stream cipher implementation that we use is the XOR algorithm. Refer to **Figure 2.2.1**. In this implementation, the keystream generator outputs a stream of bits: $k_1, k_2, k_3, \dots, k_i$. Then this keystream is XORed with a stream of plaintext bits ($p_1, p_2, p_3, \dots, p_i$) to produce the stream of ciphertext bits. This operation is described by the formula: $c_i = p_i \oplus k_i$. To recover the plaintext bits at the decryption end, the ciphertext bits are XORed with an identical keystream. This operation is described by: $p_i = c_i \oplus k_i$.

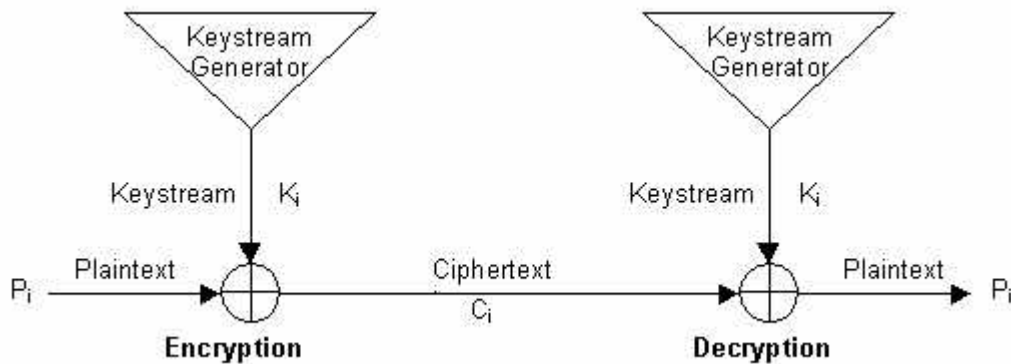


Figure 2.3.1: XOR Stream Cipher [3]

As shown in the diagram above, a keystream generator is needed. We use a keystream generator based on linear feedback shift registers (LFSRs).

The feedback shift register is made up of two parts: a shift register and a feedback function. The shift register is initialized with n bits (called the key), and each time a keystream bit is required, all of the bits in the register are shifted 1 bit to the right. So the least significant bit is the output bit. The new left-most bit is computed as the XOR of certain bits in the register. This arrangement can potentially produce a 2^n-1 bit-long pseudo-random sequence (referred to as the period) before repeating. To make this maximal-period LFSR, the polynomial formed from the tap sequence (bits that are XORed together) plus the constant 1 must be a primitive polynomial (irreducible polynomial that divides $x^{2^n-1}+1$, but not x^d+1 for any d that divides 2^n-1) mod 2. The degree of the polynomial is the length of the shift register.

Our implementation uses an 8-bit register with the primitive modulo 2 polynomial $x^8+x^4+x^3+x^2+1$. Therefore, the tap sequence consists of bit 8, bit 4, bit 3, and bit 2. By XORing these bits together, the resultant LFSR will be maximal length, so it will cycle through 2^8-1 values before repeating. Refer to Figure 2.2.2 below. Two other shift registers of length 11 bits and 13 bits are used as well. The primitive polynomials modulo 2 are $x^{11}+x^2+1$ and $x^{13}+x^4+x^3+x^1+1$, respectively.

 


Figure 2.3.2: 8-bit Long Maximal-Length LFSR [3]

By combining LFSRs of different lengths (i.e. different feedback polynomials), a keystream generator is made. To create a maximal length generator, the lengths of the constituent LFSRs must be relatively prime, and all of the feedback polynomials must be primitive modulo 2. Each time a keystream bit is required, the LFSRs are shift once and an output bit is produced as a function of the output bits of each LFSR.

The keystream generator we use is the Geffe Generator. This keystream generator uses three LFSRs combined in a nonlinear manner. Refer to Figure 2.2.3 below. Two of the LFSRs are inputs into a multiplexer, and the third LFSR controls the output of the multiplexer. Suppose a_1 , a_2 , and a_3 are the outputs of the three LFSRs, then the output of the Geffe generator is the following:

$$b = (a_1 \wedge a_2) \oplus ((\sim a_1) \wedge a_3)$$

where \wedge represents “AND”
 \oplus represents “XOR”
 \sim represents “NOT”

The period of this combination keystream generator is the least common multiple of the periods of the three generators:

$$\begin{aligned}
 n &= n_1 * n_2 * n_3 \\
 &= 13 * 11 * 8 \\
 &= 1144
 \end{aligned}$$

 


Figure 2.3.3: Geffe Generator Block Diagram [3]

This keystream generator is used at both ends – encryption and decryption.

Considering the encryption end, there are two inputs to this stage: the data to be encrypted and a clock. The data to be encrypted comes from the serial output of the previous stage. Likewise, the output from this stage is a serial output consisting of the encrypted data or ciphertext. The opposite operations occur at the decryption end. Again, there are two inputs: the encrypted data and a clock. The encrypted data is received serially from the previous stage. The output of the decryption section is the decrypted data (i.e. original message).

The stream cipher takes inputs serially and sends outputs serially. However, to interface with the other stages an 8-bit parallel-to-serial converter is required at the input and a serial-to-parallel 8-bit converter is needed at the output. When interfacing the stream cipher with the other stages, timing as well as incoming and outgoing signals are issues that must be acknowledged. To properly account for these factors, the encryption and decryption stages are considered two completely different entities, whereas before, the stream cipher designed could be used for either end without making any modifications.

The encryption stage is integrated with the analog-to-digital converter. The decryption stage is integrated with the digital-to-analog converter. There is still a similarity between the two compound entities. Both have an 8-bit shift register to convert an 8-bit parallel input to a serial stream. The shift register works in the following manner:

- i. The shift register remains in the initial (reset) stage until a data valid signal is received from the previous stage.
- ii. When a data valid signal is received, the current 8-bit parallel input is stored into the shift register.
- iii. For 8 clock cycles after receiving the data valid signal, the bits in the register are shifted such that the least significant bit (LSB) is output. During this time, the data valid out signal is asserted and output from the decryption-DAC compound entity.
- iv. After the 8 clock cycles, the output is no longer valid, so the data valid signal is deasserted.

This serial stream is then put through the stream cipher to be encrypted or decrypted. After decryption, the output data is changed from a serial stream to an 8-bit parallel output using a serial-to-parallel converter. This converter is basically a Moore finite state machine that waits for 8 valid bits (that should be received in 8 consecutive clock cycles), and then outputs these 8 bits in parallel on the next clock cycle. The finite state machine transition diagram is shown below.

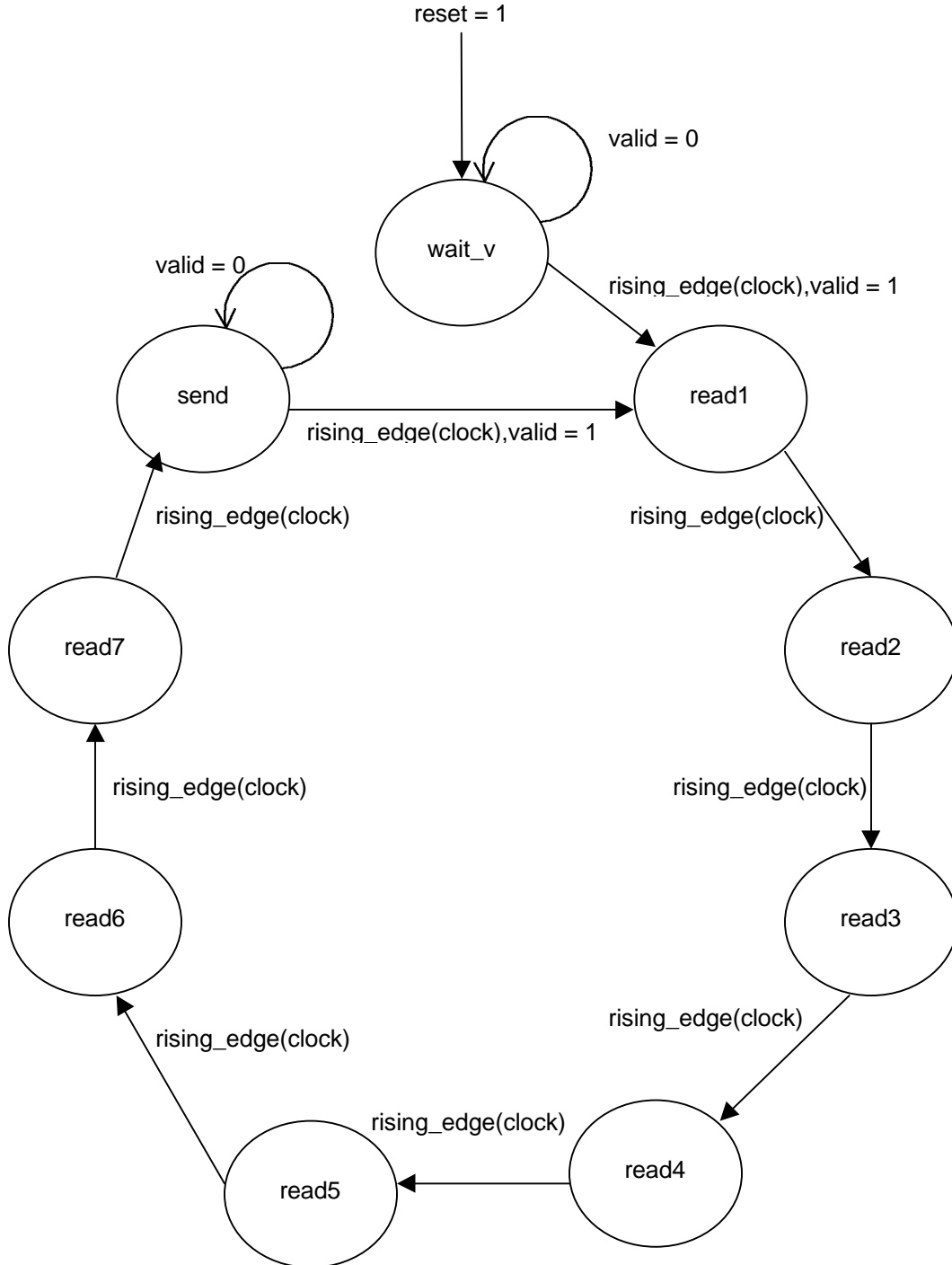


Figure 2.3.4: s_to_p_data_conv FSM Transition Diagram

The difference is that the ADC/encryption compound entity has an additional component—the ADC input reader. The way the input reader works is described in Section 2.1. There is one modification made to this component. An extra output signal, *valid_out*, is added to indicate to the encryption entity when the data being output from the ADC is valid.

Using an LFSR-based stream cipher is not considered strong encryption. The major downfall is that the key is hard-coded into the LFSRs, so the initial state of the encryption stage is always the same. The reason for its use in this project is because it is easy and fast to implement. The main concern is to get a working prototype of the SafeTalk system, even if it is a much simpler version of the one proposed. Once this is accomplished, other features such as a stronger encryption algorithm can be implemented. Ideally, a more complicated stream cipher, such as RC4, or even a block cipher, such as DES, would be implemented.

2.4 Transmitter/Receive

For the transmission stage the use of the UART can be confusing at first but is rather straightforward once an understanding of the UART is acquired. The UART is the interface between the modem and the DSP data to be transmitted/received.

This implementation of this UART transmits in blocks of 11 bits; 1 leading low start bit, 1 trailing high stop bit, 1 parity bit and 8 data bits. The UART data format is shown in **Figure 2.4.1**.

 



Figure 2.4.1: UART data format [5]

The *transmit* and *receive* line of the UART are held high while no transmission/reception is taking place. In the transmission of a sequence the active low start bit indicates to the receiving UART that a new sequence of data is on its way. This causes the receiving UART to take the next 8 bits as the transmitted data and the bit after that as the parity of these 8 data-bits. Lastly, a high stop bit is used to indicate the end of a block. The parity can be set as even or odd and is used to indicate whether or not there has been an error in the received data bits.

Note that errors can still occur even if the parity bit indicates no parity errors. For example, if the transmitted sequence is "11110000" and the parity is set as even, the parity bit that would be transmitted with the sequence would be '0'. If the received sequence is "11101000", the calculated parity of this sequence also equals the transmitted parity bit of '0', thereby fooling the receiving UART into thinking that there were no errors in transmission. To test the UART please see **Section 8**.

Note: The data is transmitted LSB first. Therefore, if "10101010" is the data to be transmitted, the transmitted/received data appears as "01010101". The whole sequence would therefore be transmitted/received in this order: "00101010101" for even parity, and "00101010110" for odd parity.

The UART module is composed of 2 modules: the transmitter (**Figure 2.3.2**) and the receiver (**Figure 2.3.3**). The operation of these two modules is not discussed here (with the exception of the baud rate clock generator), as it is not required to be able to use the UART module. For further information concerning this, refer to the UART App Notes [1] or the respective VHDL code (**Appendix E**).

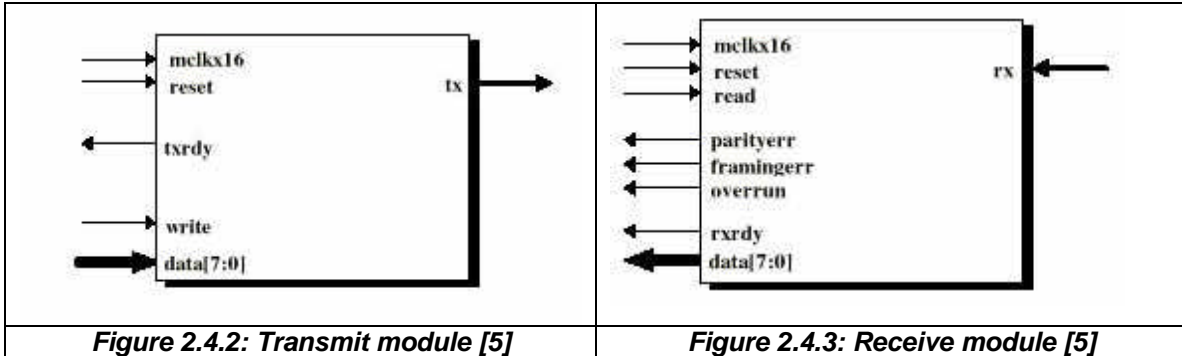

In order to use the UART you need to know what baud rate you want to transmit at. The transmitter and receiver modules have been designed with a clock divider inside, which runs 16 times slower than the clock signal sent to it. Therefore, there should be a clock divider running at 16 times the baud rate driving the UART modules.

If for example, you want to transmit at 33.6 kbps and the FPGA board runs at 25.175 MHz then:

$$\begin{aligned} \text{Baud rate} \times 16 &= 33600 \times 16 = 537600 \\ \text{Clock division ratio} &= 25175000 / 537600 \approx 46 \\ \text{Clock divisor} &= 46 / 2 = 23 \end{aligned}$$

Therefore, the clock divider used to clock the UART would be 23. This would give a transmission rate of about 34.2 kbps. Please see **Section 9** for references on clock dividers.

The implemented UART module has 12 I/O ports, which are used to control it, to get I/O to and from it, and to determine it's status. The signals and their respective descriptions are included in the **Table 2.4.1** below.

Table 2.4.1: I/O description for the UART [5]

Signal	Type	Description
mclkx16	Input	Master input clock for internal baud rate generation
reset	Input	Master reset
parityerr	output	Indicates whether a parity error was detected during the receiving of a data frame
framingerr	output	Indicates if the serial data format sent to the rx input did not match the proper UART data format
overrun	output	Indicates whether new data sent in is overwriting the previous data received that has not been read out yet.
rxrdy	output	Indicates new data has been received and is ready to be read out.
txrdy	output	Indicates new data has been written to the transmitter
read	Input	Active low strobe signal, used for reading data out from the receiver.
write	Input	Active low strobe signal, used for writing data in to transmitter.
datain(7 down to 0)	Input	Input data bus for sending/receiving data across the UART
dataout(7 down to 0)	Output	Output data bus for sending/receiving data across the UART
tx	Output	Transmitter serial output. Held high when no transmission occurring and when resetting
rx	Input	Receiver serial input. Pulled-up when no transmissions taking place.

The process of transmitting data through the UART begins by first checking the *txrdy* line. A high *txrdy* signal indicates that new data can be written to the transmitter. To write to the transmitter place the data to be transmitted on the *datain* line. The data is then latched into the UART's transmit module by a leading low signal to the *write* line. This is all that is required to transmit the data since the UART will take care of the rest. The next data sequence can be latched once the *txrdy* line goes high again.

The process of receiving data through the UART begins by waiting for the *rxrdy* line to go high. A high *rxrdy* indicates that data has been received and is ready to be read out. To read the data out from the UART's data line assert a low signal to the *read* line. This will latch the received data from the receiver to the *dataout* line allowing you to read it. The *parityerr*, *framingerr*, and *overrun* lines indicate any problems with the recently received data. The process of handling these errors will not be discussed here. Apart from this that is basically all that is required to receive data through the UART. The next data sequence received can be read out once *rxrdy* goes high again.

There are 2 FIFO buffers used. Each attached to the transmitter input and receiver output respectively. These help to keep data from being lost. The UART may not be able to transmit fast enough and as data is coming in it will probably get lost because the transmitter cannot read in values while it has not finished transmitting.

The implemented FIFO buffer has 9 I/O ports as described below in the table.

Table 2.4.2: I/O description for the FIFO [6]

Signal	Type	Description
Data	in	data port for data to be enqueued
Wrreq	in	Active high write request
Rdreq	in	Active low read request
Clock	in	clock signal
Sclr	in	synchronous reset signal
Q	output	data port for dequeued data
Full	output	Signal indicating a full FIFO
Empty	output	Signal indicating an empty FIFO
Usedw	output	Signal vector indicating number of FIFO locations used

The DSP control is the main controller for all components in the FPGA. It controls the UART, the FIFO buffers, the encryption/decryption module, the ADC and the output to the DAC. See the figure below for a better understanding.

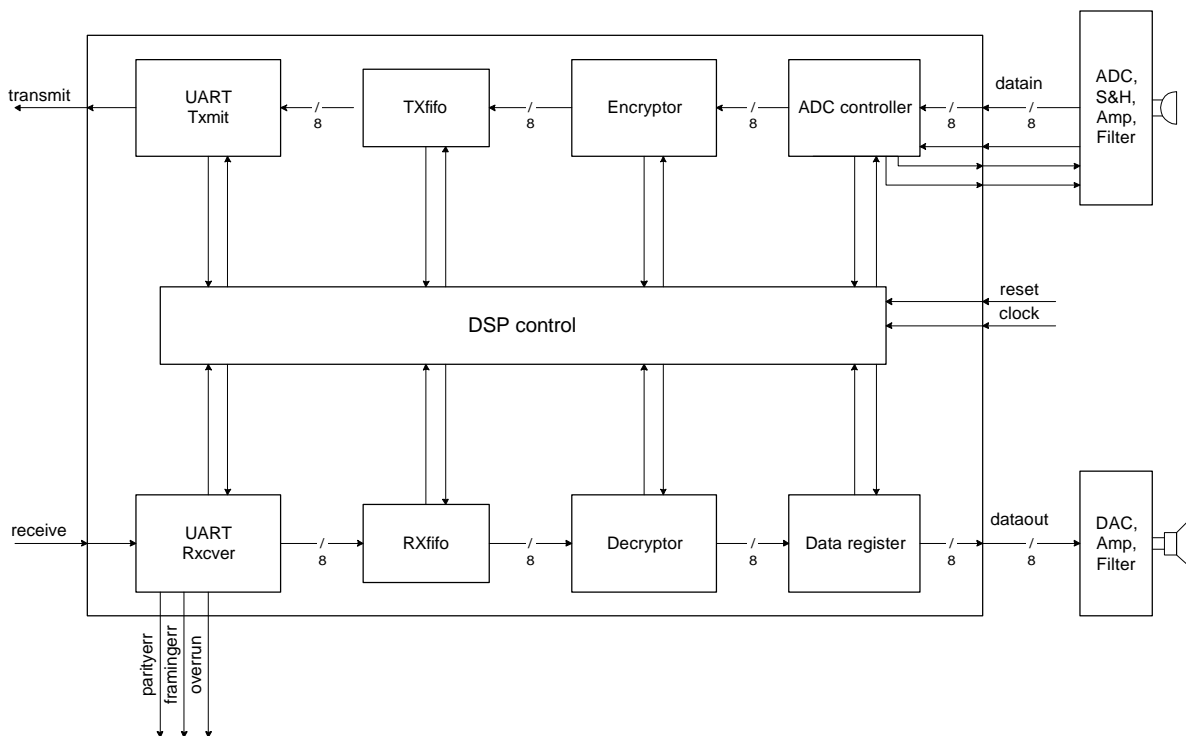


Figure 2.4.4: DSP Controller module

The ADC is the starting place. It converts the analog input from a microphone to a digital format 8-bits wide, which the encryption module takes and processes. The data is then loaded into the transmit-FIFO buffer. Once data is in the FIFO and data is ready to be sent across the transmission line, the UART transmitter module can de-queue the data.

The receiving UART module on another FPGA board receives this data and enqueue it in the receive-FIFO buffer. The decryption module takes a data block from the FIFO, decrypts it and loads it into a data register. From there the data will be output to the DAC. Please see **Sections 2.3** and **2.5** for more details on decryption and the DAC.

2.5 DAC

The Digital-to-Analog Converter (DAC) converts a digital signal to an analog form. The DAC designed in this project receives an 8-bit digital data and outputs an analog signal. Theoretically speaking, the analog signal output from the DAC has to be similar to the analog signal input except for some signal delay, amplification and noise interference.

For the hardware design the circuit is divided up into the four different sub-sections as follows:


1. D/A Converter (DAC0806)
2. Operational Amplifier
3. Low Pass Filter (LF 351)
4. Speaker

The D/A converter is an 8-bit monolithic DAC chip which converts an 8-bit digital input into an analog current. The 8-bit input data ranges from '00000000' to '11111111' (in binary) which is equivalent to a range of 0 to 255 (in decimal). The LF351 is a JFET input operational amplifier then converts these currents into analog voltage V_{out} . The range of the V_{out} is from 0V to 9.96V for $V_{ref} = 10V$ according to the equation below:

$$V_{out} = V_{ref}(A1/2 + A2/4 + A3/8 + A4/16 + A5/32 + A6/64 + A7/128 + A8/256) \text{ where } V_{ref}=10V$$

The schematic diagram of the DAC is as shown in the diagram below. The design of the DAC is taken from the specification sheet of DAC0808.

Figure 2.5.1 : Block Diagram of DAC

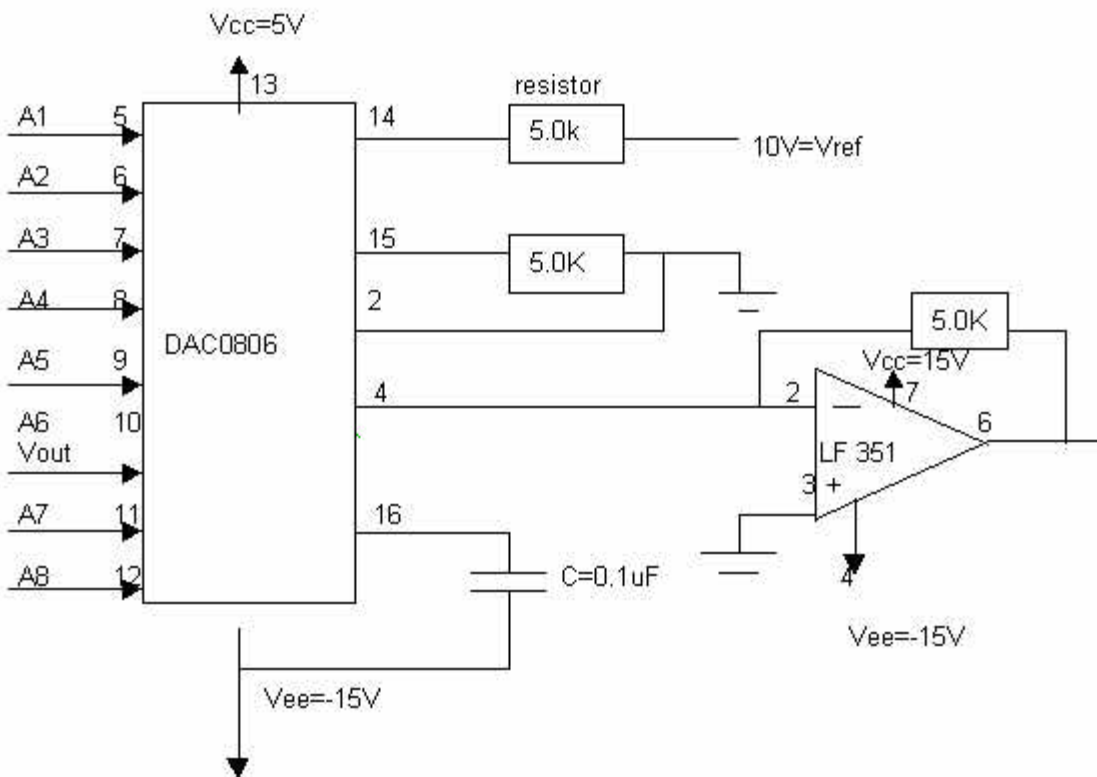

Design of the Low-pass filter:

The low-pass filter provides an input signal that contains no frequency components above the cutoff frequency of the filter. The cutoff frequency is the maximum frequency passed by the filter. A simple low-pass filter can be implemented by an RC circuit [2]. A simple RC circuit low-pass filter is shown below.

 


Figure 2.5.2: Low-Pass filter

In telephone communication, the components above 3000Hz are eliminated by a low-pass filter [4].

Therefore, if the cutoff frequency, B of the low-pass filter is equal to 3000Hz, for the RC circuit:

$$CR = \frac{1}{\omega_o} \text{ for a DC gain of one}$$

$$CR = \frac{1}{2\pi B} = 5.305e-05$$

$$\text{For } C = 0.1\mu\text{F}, R = 530\Omega.$$

The block diagram of the entire design of the DAC with a low pass filter to eliminate noise interference is shown in the diagram below:

 


Figure 2.5.3: DAC Block Diagram

2.6 DSP Control

There are inherent delays between each stage, therefore it is necessary to have a controller to direct the flow of data. This is made possible by the control signals present in each of the modules. The controller supervises and directs the flow of data through these signals so that no loss of data occurs. With the exception of the ADC, the encryptor/decryptor modules the remaining modules are clocked at the baud rate clock (which is at 16x the desired baud rate) which is running at a speed of about 1.4 MHz. This translates to a baud rate of about 87.42 kbps. The encryptor/decryptor are clock at the speed of the FPGA to reduce the amount of overall delay. A summary of the control signal from each module is shown in the table below.

Table 2.6.1: Module control signals

Module	Control signals
Encryptor/Decryptor	valid_in, valid_out
FIFO	wrreq, rdreq, full, empty, usedw
UART	read, write, rxrdy, txrdy, parityerr, framingerr, overrun

The encryptor loads and starts encrypting the current data from the ADC once the ADC module's *valid_out* signal goes high. When encryption has been completed the encryptor's *valid_out* signal switches high signaling the controller that the data can be loaded into the transmit FIFO. The last step for transmission is for the UART to send the data out it's *transmit* line. This is done when the FIFO is not empty and the UART is ready to transmit (i.e. *empty* = '0' and *txrdy* = '1').

The reception of the data is controlled in a similar manner. The transmitted data is received at the receiving UART, which loads the received data into the receiving FIFO. The controller then loads the data from the FIFO to the decryptor, which decrypts the data and outputs it to a data register. The data register is connected to the output, which goes directly to the DAC. The data register is used to hold the data steady and at a correct value so that the DAC gets the correct data.

Synchronization is taken care of by the very nature of the design. This is because each module is dependent on the data and control signals sent to them from the DSP control. The DSP control enables each module in succession, as valid data becomes available. On the power up of the system, the controller disables all modules. The FIFO would not load any data since the DSP control would not let it until valid data arrives. Since no data is getting to the transmitting UART, the receiving UART does not receive any data and therefore would not send any invalid data through the DSP modules to the DAC. Once valid data from the ADC is transmitted to the FPGA, processing can commence and the UART can start sending valid asynchronous data. Adding a modem to transmit the data over a phone line shouldn't affect this procedure in any way. The modem just modulates the signal so that it can be transmitted through the phone line and does not change the transmitted data in any way.

3. I/O Signals

3.1 ADC

For the input and output descriptions, we will start with the 4 main components of the A/D followed by the input and output description of the entire circuit. The 4 major components used in the A/D design are as follows:

1. LM324
 2. LF 351
 3. SMP11
 4. ADC0809
- ◆ The LM324 chip consists of four independent, high gain, internally frequency compensated operational amplifiers which are designed specifically to operate from a single power supply over a wide range of voltages. The table below illustrates the input and output pin connections of the chip.

Table 3.1.1: LM 324 Chip I/O Pins

Lines	Pin Number (s)
Output1	1
Input1 ⁻	2
Input1 ⁺	3
Output4	14
Input4 ⁻	13
Input4 ⁺	12
Power Supply (V+)	4
Gnd	11

- ◆ The LF 351 chip is a low cost high speed JFET input operational amplifier with an internally trimmed input offset voltage (BI-FET II™ technology). The device requires a low supply current and yet maintains a large gain bandwidth product and a fast slew rate. The LF351 is pin compatible with the standard LM741 and uses the same offset voltage adjustment circuitry.

The LF351 may be used in applications such as high speed integrators, fast D/A converters sample-and-hold circuits and many other circuits requiring low input offset voltage, low input bias current, high input impedance, high slew rate and wide bandwidth. The device has low noise and offset voltage drift.

Table 3.1.2: LF 351 Chip I/O Pins

Lines	Pin Number (s)
Output	6
Input ⁻	2
Input ⁺	3
Power Supply (V-)	6
Power Supply (V+)	7

- ◆ The SMP-11 is precision sample-and-hold amplifiers that provides high accuracy, a low droop rate, and the fastest acquisition time required in data acquisition and signal processing systems. The SMP-11 is essentially a non-inverting unity gain circuit consisting of two very high input impedance buffer amplifiers connected together by a diode bridge switch.

The sample-time and hold characteristics are provided in the specification sheets in the Appendix together with a complete diagram of the pin connections. The table below states the input/output lines and their corresponding pin numbers:

Table 3.1.3: SMP-11 Chip I/O Pins

Lines	Pin Number (s)
Input	2
Output	7
Voltage Source (+ve)	9
Voltage Source (-ve)	5
Hold Capacitor (C_H)	11
Logic Control, V_{LC}	13
S & H Control	14
Null Input Offset	3, 4

- ◆ The ADC0809 is a 28-pin “skinny” DIP chip with MUX made by National Semiconductor. The ADC0809 offers high speed, high accuracy, minimal temperature dependence, excellent long-term accuracy and repeatability, and consumes minimal power. The table below states the input/output lines and their corresponding pin numbers:

Table 3.1.4: ADC0809 Chip Input Pins

Lines	Pin Number
Input0	26
Input1	27
Input2	28
Input3	1
Input4	2
Input5	3
Input6	4
Input7	5
Input Select	25,24,23
SOC (start conversion)	6
Output enable	9
Address latch enable (ALE)	22
Clock	10

Table 3.1.5: ADC0809 Chip Output Pins

Lines	Pin Number
Output (2^{-1}) *MSB	21
Output (2^{-2})	20
Output (2^{-3})	19
Output (2^{-4})	18
Output (2^{-5})	8
Output (2^{-6})	15
Output (2^{-7})	14
Output (2^{-8}) *LSB	17
Conversion Done Signal (EOC)	7

Space Intentionally Left Blank

3.4 DAC

The tables below show all the pin numbers for the DAC 0806 and LF351

Table 3.4.1: DAC0806 Input pin numbers

Digital Input Line	Pin number
A1	5
A2	6
A3	7
A4	8
A5	9
A6	10
A7	11
A8	12

Table 3.4.2: DAC0806 Pin Label

Lines	Pin number
Vcc (power supply voltage 5V)	13
Vee (power supply voltage -15V)	3
Vref(+) reference voltage	14
Vref(-) reference voltage	15
GNC	2
Io(output)	4
NC(note2)	1
Compensation	16

Table 3.4.3: Pin Label for LF351

Pin Label	Pin number
Input(-)	2
Input(+)	3
V- (Vee=-15V)	4
NC	8
V+ (Vcc=15V)	7
Output(Vout)	6
Balance	1, 5

Below is the schematic wiring diagram of the chips DAC 0806 and LF351:

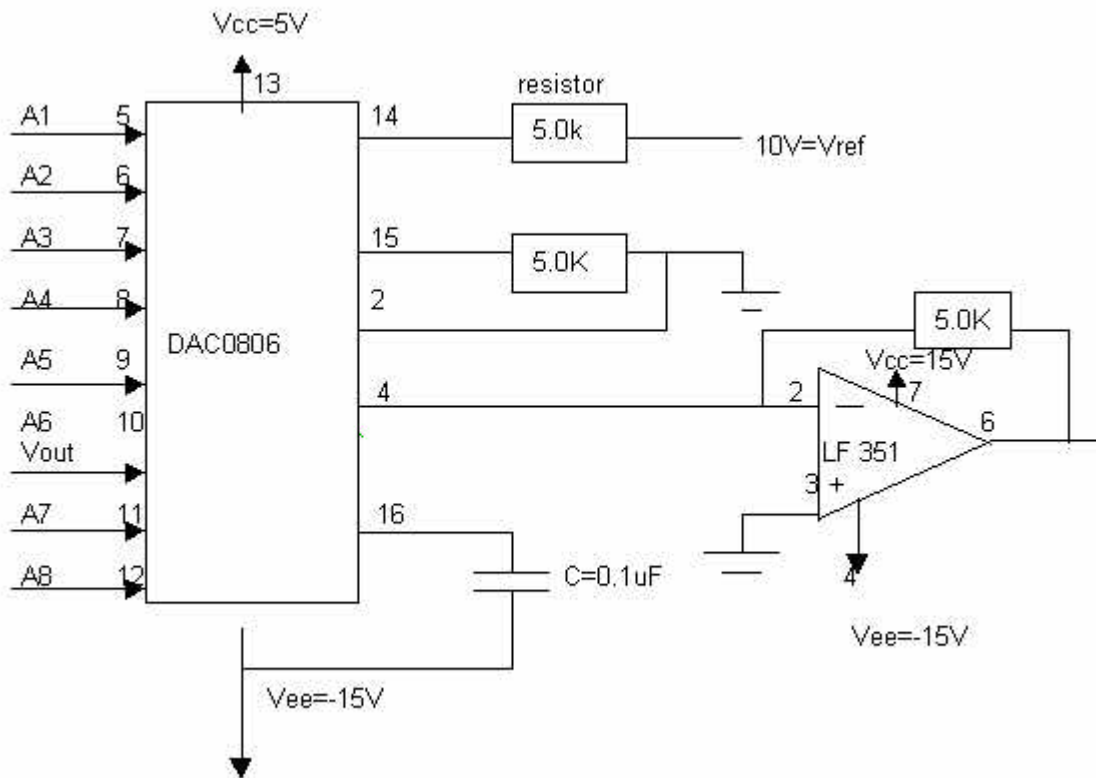


Figure 3.4.1: +10V output Digital to Analog Converter Schematic [1]

The analog voltage samples a staircase waveform from the D/A converter. A low-pass filter then filters this waveform, and the result is a smooth waveform.

4. Design Hierarchy

The overview of the VHDL entities of SafeTalk is shown in **Figure 3.1**. Basically, the SafeTalk design consists of a controller that controls all the entities of the sub-sections. The controller is essential to the design since some of the entities run on different clock frequencies and hence, we need the controller to provide synchronism.

The Encryption/Decryption module is broken up into two stages. See figure 3.3.1


1. ADC & Encryption
 - *adc_cipher_connect.vhd* (interfaces the ADC hardware with the encryption algorithm)
 - *input_reader.vhd*
 - *stream_cipher.vhd*
2. Decryption & DAC (interfaces the DAC hardware with the decryption algorithm)
 - *dac_cipher_connect.vhd*
 - *stream_cipher.vhd*

The UART Transmit module is broken up into one stage.

1. txmit – responsible for transmitting data and ensure proper framing and data parity

The UART Receive module is broken up into one stage.

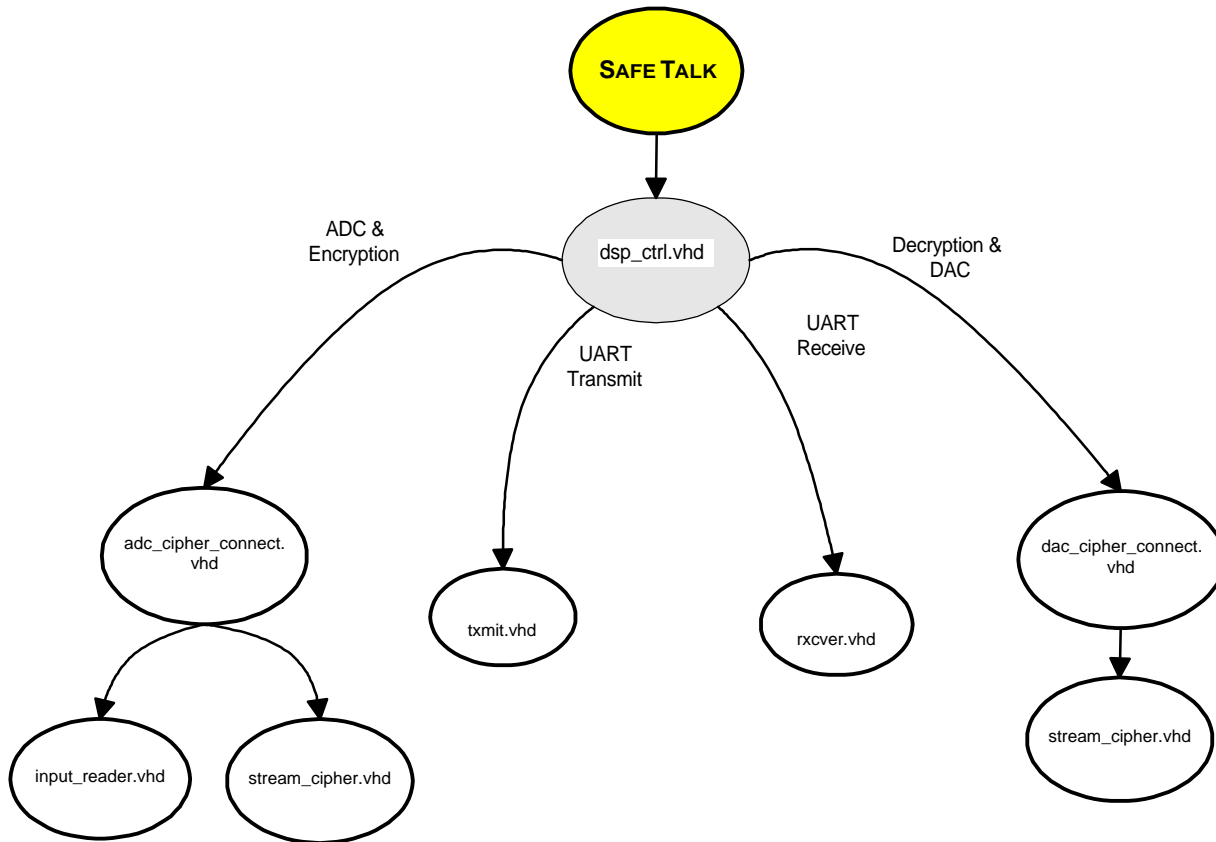1. rxcvr – accepts correct data from UART transmitter. See **Section 2.3** for details.



Note : All VHDL codes stated above compiles without errors or bugs.

Figure 4.1: Design Hierarchy

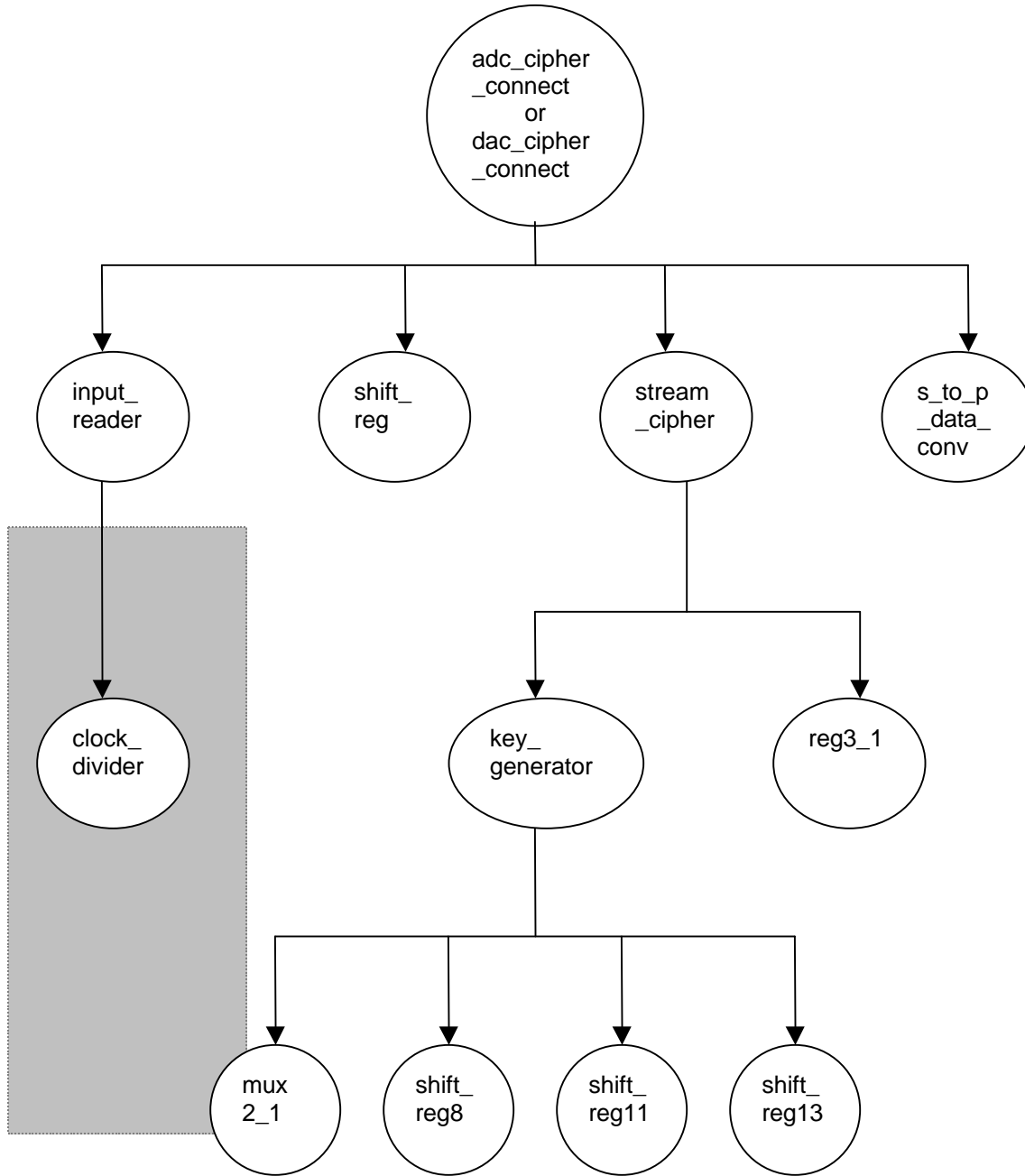


Figure 4.2.1: ADC/Encryption & Decryption/DAC Hierarchy

Note that the shaded part is included in the `adc_cipher_connect` entity but not the `dac_cipher_connect` entity.

5. FPGA Resources

5.1 ADC

The logic cells required for each component in the ADC is given below:

Table 5.2.1: Logic Cells for Encryption/Decryption

Component	Number of Logic Cells Used
clock_divider (ADC)	6
input_reader (ADC)	30

5.2 Encryption/Decryption

The logic cells required for each component in the stream cipher is given below:

Table 5.2.1: Logic Cells for Encryption/Decryption

Component	Number of Logic Cells Used
Shift_reg	39
S_to_p_data_conv	38
Stream_cipher	38

Combining these components (and in the case of encryption, the ADC components) the higher level entities require the number of logic cells listed below:

Table 5.2.2: Logic Cells for Encryption/Decryption

Entity	Number of Logic Cells Used
adc_cipher_connect	138
dac_cipher_connect	113
Total	251/1152 (22%)

5.3 Transmitter/Receive

The logic cells required for each component in the transmitter/receive is given below:

Table 5.3.1 Logic Cells for Tx/Rx

Entity	Number of Logic Cells Used
UART	78
FIFO (2)	486
Total	564/1152 (49%)

<p>Total logic cells used: 886/1152 (76%) (dsp_ctrl.vhd – including all components)</p>

6. Experimentation

6.1 Transmitter/Receive

Experiments were performed to test the different transmission rates that are attainable. Three different rates were tested as listed below.

- Baud rate of 98.3kbps framing and parity errors occurred.
- Baud rate of 87.4kbps framing and parity errors also occurred.

It was found that although simulations showed that this rate was attainable, real life testing on the FPGA proved differently

The UART receiver module would not receive properly on the FPGA board but simulated properly in MAX+Plus II. With experimentation we were able to get the FPGAs to receive the transmitted data without any framing or parity errors. At first it was suspected that the transmission speed was set too high. This was not the case after testing it at lower speeds of about 9600 bps. We know that the UART transmits the start bit then the data with the LSB first. What we discovered is that if the LSB is a zero the receiver will not receive correctly. On the other hand, if the LSB is a one the data is received correctly. This finding allowed us to transmit and receive correctly by setting the LSB as always one. This does not affect the sample since it is at the LSB position. The difference between a one or a zero in the LSB would not change the analog signal by very much. This would not be the case for the MSB.

The FIFO buffers that we used are 16x8-bits. This took up 243 logic cells, which is quite a large number. We tried to reduce this by decreasing the size from 16 to 8 but that only decreased the overall usage of logic cells by about 30. As a result we decided to stay with a 16 level FIFO.

6.2 Compression/Decompression

The compression and decompression modules were researched extensively and with the help of Dr. Elliott an algorithm that breaks down the audio signal into high frequencies and low frequencies. **Figure 6.2.1** shows how this breakdown occurs. As well the following logic of how this is implemented is shown in **Figure 6.2.2**.

 


Figure 6.2.1: Breakdown of 8-bit digital signal (compression)

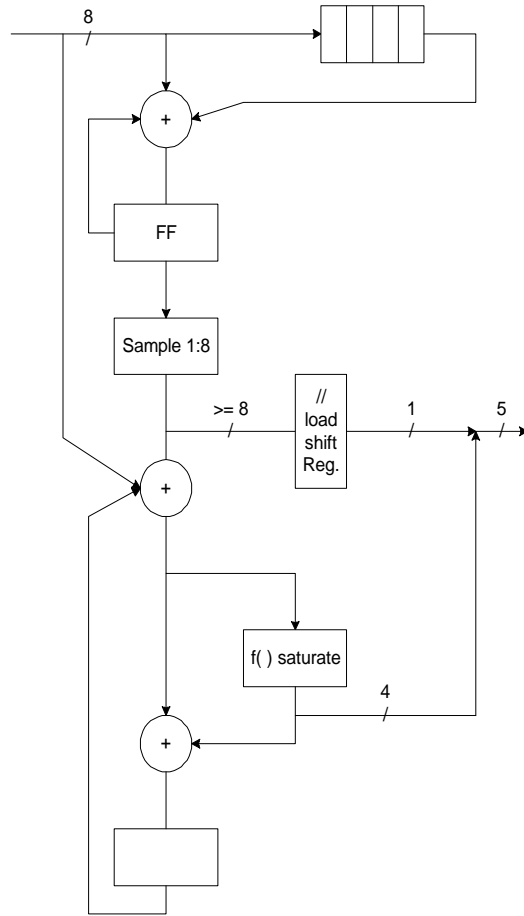


Figure 2.5.2: Automatic Gain Adjuster

The design of the automatic gain adjuster was suggested to us by Dr. Elliott for use in the compression of the digital speech signal. **Figure 2.5.2** shows the gain adjuster with the low frequency bits sampled at 1 in every 8 normally sampled bits, and 4 bits for every high order bits.

8. Research

8.1 Compression/Decompression

Compression and decompression of an audio signal is not used in SafeTalk for several reasons that were researched and due to a lack of time was not implemented. The conversion of an audio signal from analog to digital is simple however the data that results in the digital signal is large compared to the data needed to reconstruct it and convert it back to analog. As a result a large speed modem—64Kbps—would be required to send all the information. This modem speed could not be obtained therefore compression is needed. Several algorithms were researched and are reported below for the reasons why they were considered and why they were rejected.

The members did not have any basis as to how compression worked, and therefore research started at the search engines on the Internet. The progression of compression knowledge started with file data compression—lossless compression—and turned to adaptive differential pulse code modulation (ADPCM) with A-law and Mu-law—lossy compression. The group assumed that compression of an audio signal was researched before, therefore, research continued for longer periods than reasonable for this project.

Arithmetic coding is a function of the probability of a digital sample and its encoding interval range. This compression takes a value and gives it a range that is between 0 and 1. The way arithmetic encoding works is that each 8-bit digital value is given a probability—for example 00000000 has a 10% probability of showing up. Next this probability would be given an interval—in the range from 0 to 1. The problem with this is that using digital logic we could not get the interval to break up into 256 segments nicely. Although consideration was given to developing a different range value, the assumption was that other algorithms were already developed and this would require more work that was needed.

Run-length Coding was looked at as being a viable compression technique. It works best with redundant data that is repeated, and initially voice seemed to be something that was repeated enough that this could be used. The reason for this assumption was because the sample rate was very high—8KHz—so in terms of the sample rate being much, much higher than an average speech sample the redundancies could be reduced using this algorithm.

It turns out that this lossless algorithm could not be used because of the nature of audio sample. As well, the 8-bit sample does not have many redundant bits—as images might have; therefore the run-length encoding was disregarded.

A form of compression—called dictionary method—uses combinations of data and represents this as a smaller section of data. On the Internet various algorithms were found, and in particular the Lempel-Ziv algorithms were considered. This is a lossless algorithm that seemed the best case, and steps were taken to deepen the understanding of LZ algorithms. A version of LZ is called LZA seemed the most likely because the decompression time was virtually zero, so with the delay that we had in transmission, this was the first compression technique that started. C code was available for this and the initial compilations took place.

It was then pointed out that this was a lossless compression technique and lossless was not needed for audio compression.

Baffled at this point, a small investigation of how people in general perceive speech. What was found was that at high frequencies—above 2KHz—the human ear uses envelope detection. This was good to know, considering the sampling rate could reconstruct signals that were up to 3.5KHz. Digital data that was changing faster than 2KHz might not need to be accurate to reconstruct the exact signal.

In continuing with research, Dr. Elliott introduced a method that utilized dynamic amplifier control. The way the algorithm works is that the audio signal is separated into high amplitude and low amplitude. The most significant bits (MSB) of the 8-bit audio signal dominate the high amplitudes. Likewise the least significant bits dominate the lower amplitudes. These two modes can be signified with a switch so that when people are going to shout then the higher 4 bits could be used. The resulting bits over a modem would be $4\text{bits/sample} * 8000\text{ sample/sec} = 32\text{Kbps}$, which could work over a phone line.

9. References

- [1] DAC data sheet : <http://www.national.com/pf/DA/DAC0808.html>
- [2] Microelectronic Circuits by Sedra/Smith
- [3] Bruce Schneier, "Applied Cryptography", 2nd edition, John Wiley & Sons, Inc., 1996
- [4] Modern Digital and Analog Systems by B.P.Lathi
- [5] QuickLogic's Application Notes and QuickNotes
<http://www.quicklogic.com/support/anqn/>
(Digital UART Design Using Hardware Description Language)
<http://www.quicklogic.com/support/anqn/an20.pdf>
- [6] MAX+Plus II v9.23
MegaWizard Plug-In Manager
- [7] EE 552 Student Application Notes

10. Test Case Index

This section of the report basically describes all the test cases and simulations performed on all the sub-sections.

10.1 ADC

Test case 10.1.1:

Simulation of *input_reader.vhd* under normal conditions.
Set *EOC* = '1' - End of conversion hence continue proceeding to next state of finite state machine. Set *nreset* = '1' - No reset wanted for this test case. Focus observation on *next_state* that runs from one state to the other continuously on the simulation waveform.

Test Case 10.1.2:

Simulation waveform when the *EOC* signal is set to zero in the middle of the conversion i.e. conversion is not done yet. Focus observation on *next_state* of simulation waveform. State remains at state 2 as long as the *EOC* signal is zero. State resumes to state 3 when *EOC* is set to one.

Test Case 10.1.3:

Simulation waveform the signal *EOC* is set to zero for the entire duration. Focus observation once more at *next_state*. State remains at state 2.

Test Case 10.1.4:

Simulation waveform when reset is set to zero. Note that reset is active low. Focus observation on *next_state* that returns to the initial state, *sample_conv* when the *nreset* signal is low.

Test Case 10.1.5:

For testing purposes of *clock_divider.vhd*, we will set the divisor value to 1. This will decrease the normal clock period rate by a factor of 2 times.

Test Case 10.1.6:

The ADC and DAC are connected together. A function generator is used to produce an input to the system. Output waveform is identical with the input waveform.

Test Case 10.1.7:

The ADC and DAC are connected together. An analog voice signal is used as an input through a microphone, and the output is observed on the oscilloscope and heard through the speakers. Output waveform is similar to the input waveform except for some amplification and noise interference.

10.2 Encryption/Decryption

Test Case 10.2.1:

All three LFSRs are tested in the same manner. Each LFSR is seeded with a hard-coded key, the enable line is always high, and a clock with a 20.0ns period is used. After every clock cycle, the LFSR outputs one bit. The value of this bit, as well as the value stored in the register, is compared with the results obtained by hand.

Test Case 10.2.2:

During simulation of the keystream generator, the enable line is always high and the clock has a period of 20.0ns. After every clock cycle, the keystream generator outputs one bit. The value of this bit is compared with the results obtained by hand.

Test Case 10.2.3:

The stream cipher is simulated. Plaintext bits feed serially into one input of the register, and the keystream feeds serially into the other register input. The register latches 1 bit from each input at the rising edge of every clock cycle. Then the two bits are XORed to produce a ciphertext bit. The output is compared with the results obtained by hand.

Test Case 10.2.4:

The complete stream cipher (with the serial-to-parallel converter) is simulated. Inputs are fed serially, the encrypted output is sent 8 bits in parallel.

10.3 Transmitter/Receive

Test Case 10.3.1:

Transmit module testing (*txmit.vhd*)

The testing of the transmitter was done by sending the transmitter the required signals and data. Once the parallel input data of the transmitter module is sent out of the serial line, the two values can be compared for validation. During the testing of the transmit module the baud rate clock was set to divide the master clock by 4.

Test Case 10.3.2:

Receive module testing (*rxcvr.vhd*)

The testing of the receiver module was similar to the testing of the transmitter module.

Test Case 10.3.3:

DSP module testing (*dsp_ctrl.vhd*)

The testing of the DSP control transmitter was done by giving it parallel input of 6 different values. The serial output obtained were then compared to the parallel input values to ensure proper transmission has taken place.

Test Case 10.3.4:

The testing of the DSP receiver control was similar but with the input as serial and the output as parallel. The inputs were compared to the outputs to determine the validity of the reception.

Test Case 10.3.5:

Testing of the entire project began with the simulations. The sub-components including the ADC controller, the encryption/decryption, and transmission/reception are all connected appropriately. Testing of the project was similar to testing the dsp controller without the encryption/decryption. With the added encryption/decryption modules, which are clocked at a different speed than the other modules, careful attention has to be considered concerning timing issues. With the testing through simulations, it was verified that the project works as it should.

10.4 DAC

Test Case 10.4.1:

A simple VHDL program that provides an 8-bit digital input to the DAC by using switching is used. Each switch represented different input bit. Therefore, when all the switches were on, the digital input of the DAC would be 11111111. The result voltage V_{out} from the LF351 would be equal to $V_{out} = 10V(1/2 + 1/4 + 1/8 + 1/16 + 1/32 + 1/64 + 1/128 + 1/256) = 9.96V$ according the formula that given from the datasheet of the chips.

Test Case 10.4.2:

An 8-bit counter is used to produce digital inputs for the DAC. The counter is constructed by VHDL code. The program produces 8-bit binary numbers to input to the DAC. The counter counts up from 0 to 255 and then counts down from 255 back to 0. Again the results are compared with the values determined by the V_{out} formula.

Test Case 10.4.3:


The ADC and DAC are connected together. A function generator is used to produce an input to the system. Output waveform is identical with the input waveform.

Test Case 10.4.4:

The ADC and DAC are connected together. An analog voice signal is used as an input through a microphone, and the output is observed on the oscilloscope and heard through the speakers. Output waveform is similar to the input waveform except for some amplification and noise interference.

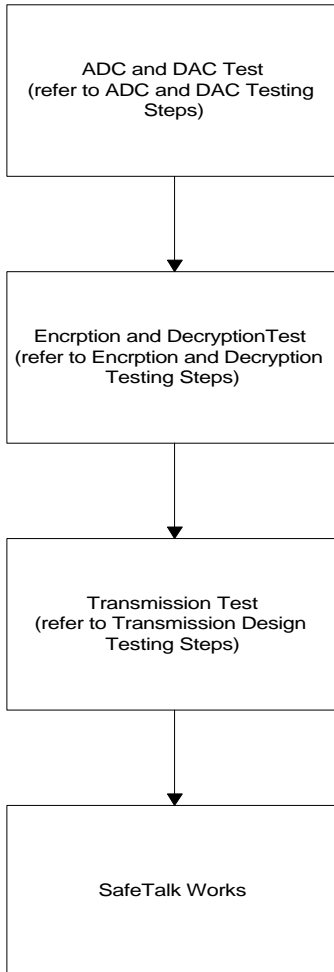11. Design Verification

To provide a concise explanation of the sequential steps performed to the various sub-sections, the flowchart below depicts clearly the overall process:




Testing Steps of Overall Project

11.1 ADC

The flowchart below describes the sequential testing cases for the ADC and DAC:

ADC and DAC Testing Steps

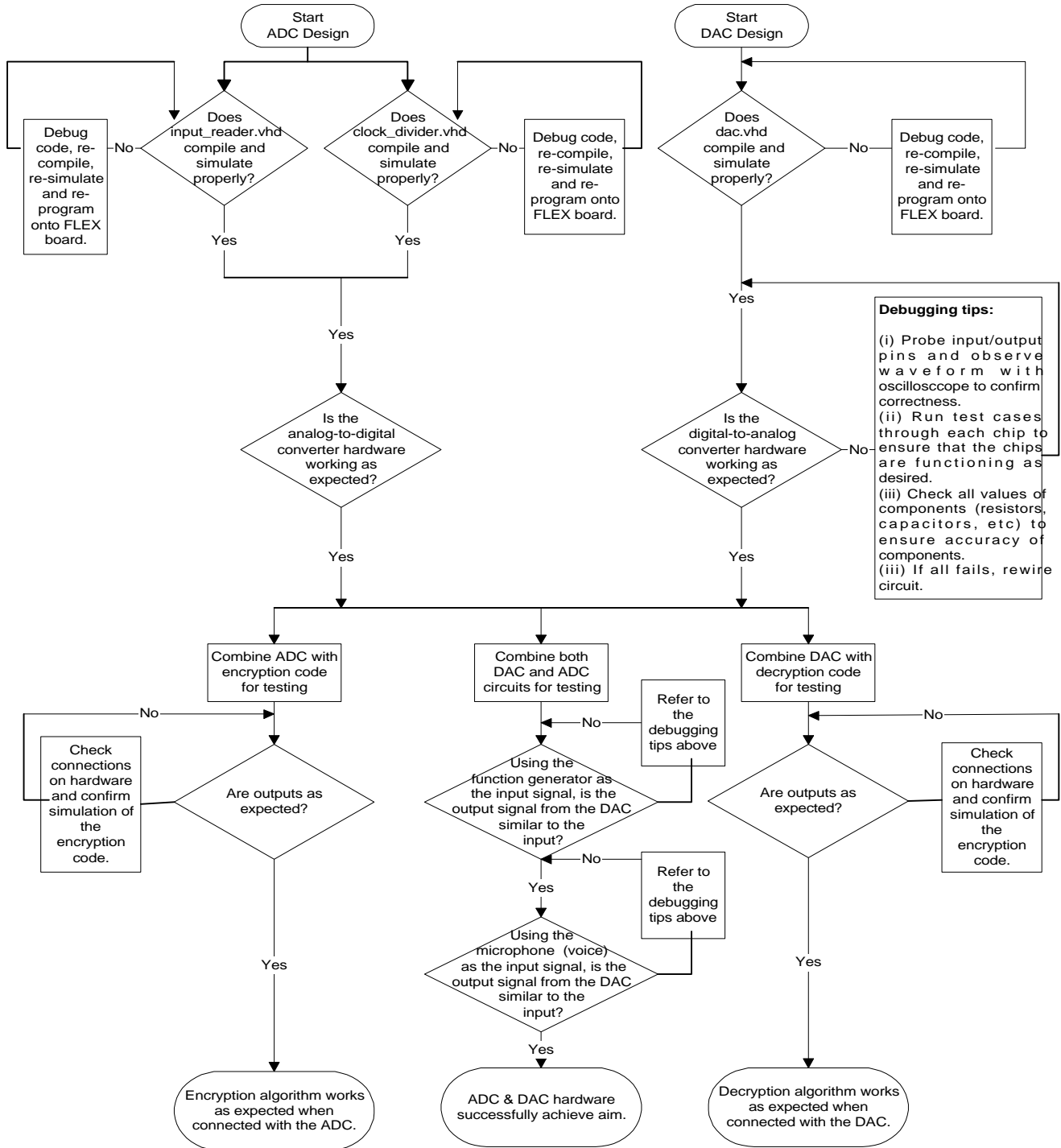

11.1.1 Testing the Hardware

Connect the hardware to the function generator as the input waveform. Assign the pin assignments on the FLEX20K board as follows:

Signal	Pin Number	Hole Number	Signal	Pin Number	Hole Number
Bit(0)	55	23	Data_out(0)	72	35
Bit(1)	56	24	Data_out(1)	73	36
Bit(2)	61	25	Data_out(2)	74	37
Bit(3)	62	26	Data_out(3)	74	38
Bit(4)	63	27	Data_out(4)	76	39
Bit(5)	64	28	Data_out(5)	78	40
Bit(6)	65	29	Data_out(6)	79	41
Bit(7)	66	30	Data_out(7)	80	42
Nreset	-	28	Sample	83	45
NEOC	81	43	Slow_clock	101	56
SOC	82	44	Gnd	Gnd	60

Then, the frequency desired is adjusted. The desired amplitude can also be fixed. Probe the EOC, SOC, sample and the clock signal with the oscilloscope probe. Observe waveform on the oscilloscope.

Finally, the divisor value on the VHDL code *clock_divider.vhd* is changed. Increasing the divisor would mean that the blinking of the LEDs would be faster. Decreasing it makes the LED blinks really quickly.

Results

Output waveform is similar to the input waveform generated by the function oscillator for all cases. Circuit testing a success.

11.1.2 Testing the VHDL code *clock_divider.vhd*:

Using the divisor value of 2, the *slow_clock* will be 2 times slower than the regular clock.

Results:

Slow_clock waveform is indeed slower than the period of clock by 2 times.

11.1.3 Testing the VHDL code *input_reader.vhd*:

Test case 1:

Waveform 1: Simulation under normal conditions.

Set *EOC*='1'- End of conversion hence continue proceeding to next state of finite state machine. Set *nreset*='1'- No reset wanted for this test case. Focus observation on *next_state* that runs from one state to the other continuously on the simulation waveform (as expected).

Test Case 2:

Waveform 2: Simulation waveform when the EOC signal is set to zero in the middle of the conversion i.e. conversion is not done yet. Focus observation on *next_state* of simulation waveform. State remains at state 2 as long as the EOC signal is zero. State resumes to state 3 when EOC is set to one.

Test Case 3:

Waveform 3: Simulation waveform the signal EOC is set to zero for the entire duration.
Focus observation once more at *next_state*. State remains at state 2.

Test Case 4:

Waveform 4: Simulation waveform when reset is set to zero. Note that reset is active low.
Focus observation on *next_state* that returns to the initial state, *sample_conv* when the *reset* signal is low.

Results:

All results of the 4 waveforms are as expected. Code *input_reader.vhd* is correct.

11.1.4 Testing the ADC with DAC hardware:


Combining the A/D to the D/A, we used the function generator as an input waveform going into the A/D. The outputs produced by the D/A circuit are exactly similar to that of the input waveform produced by the function generator. The clock frequency used was approximately 840kHz. This is due to the design limitations of the DAC circuit. Listed below are some of the test cases done using the function generator:

The plots below illustrate the waveforms observed from the oscilloscope:


	Frequency of the Input Waveform (Hz)	Input Voltage into ADC ($V_{\text{peak-to-peak}}$)	Period of Waveform into ADC		Output Voltage received at DAC ($V_{\text{peak-to-peak}}$)	Period of Waveform from DAC		Time delay of the output from DAC (phase shift between the input and output)
			(Hz)	(ms)		(Hz)	(ms)	
1	10	1	10	100	4.76	10	100	384.6Hz(2.6ms)
2	100	1	100	10	2.88	100	10	90.91Hz(11ms)
3	1000	1	1000	1	1.02	1000	1	2kHz(500us)

The plots below illustrate the waveforms observed from the oscilloscope:


Trial 1:

 

Trial 2:

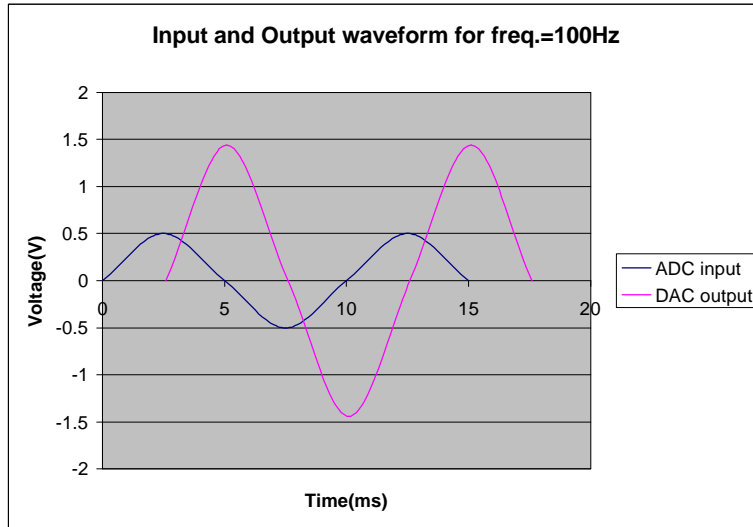

Trial 3:

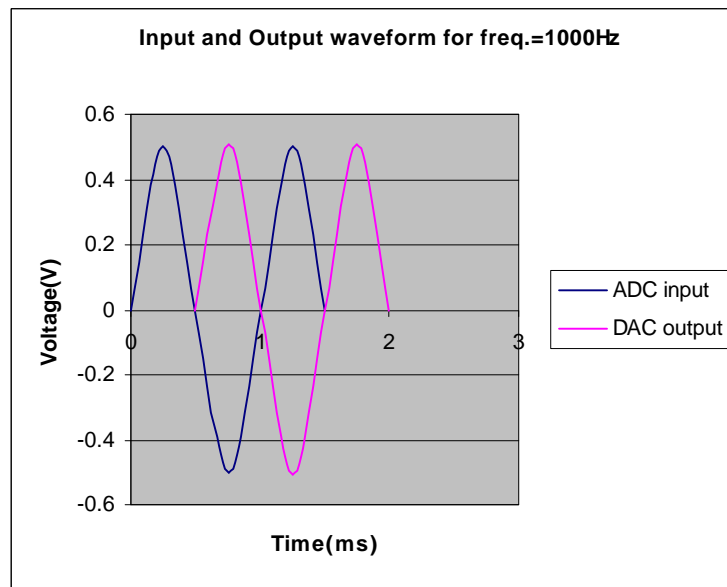


Note : These graphs are plotted using MicroSoft Excel and the waveforms (lines) produced are very much more fine than the ones observed on the oscilloscope. Due to noise interference and other disturbances that occurred with the input signal, the sinusoidal waveform seen on the oscilloscope is courser and 'dirtier' than the ones plotted using Excel.

The amplitudes of the input signal for the test cases 1 are fixed equal to 1V_{peak-to-peak}. The input and output waves are tested by probing the signals with the oscilloscope probe. The amplitude of the output voltage is greater than the input wave due to the fact of the amplifier. The waveform shows that the frequency of the output waveform is the same as the input wave. However, there is a phase shift between the input and output signal, it was found that the phase shift is due to the time delay of the output and the delay became larger as the input signal frequency increased. Test cases was performed up to 1000Hz due to limitations of the ADC circuit. All of the input signals

with frequency greater than 3KHz will cutoff since the low-pass filter in the DAC was designed to have a cut-off frequency of 3000Hz which is the bandwidth used in telephone communications.

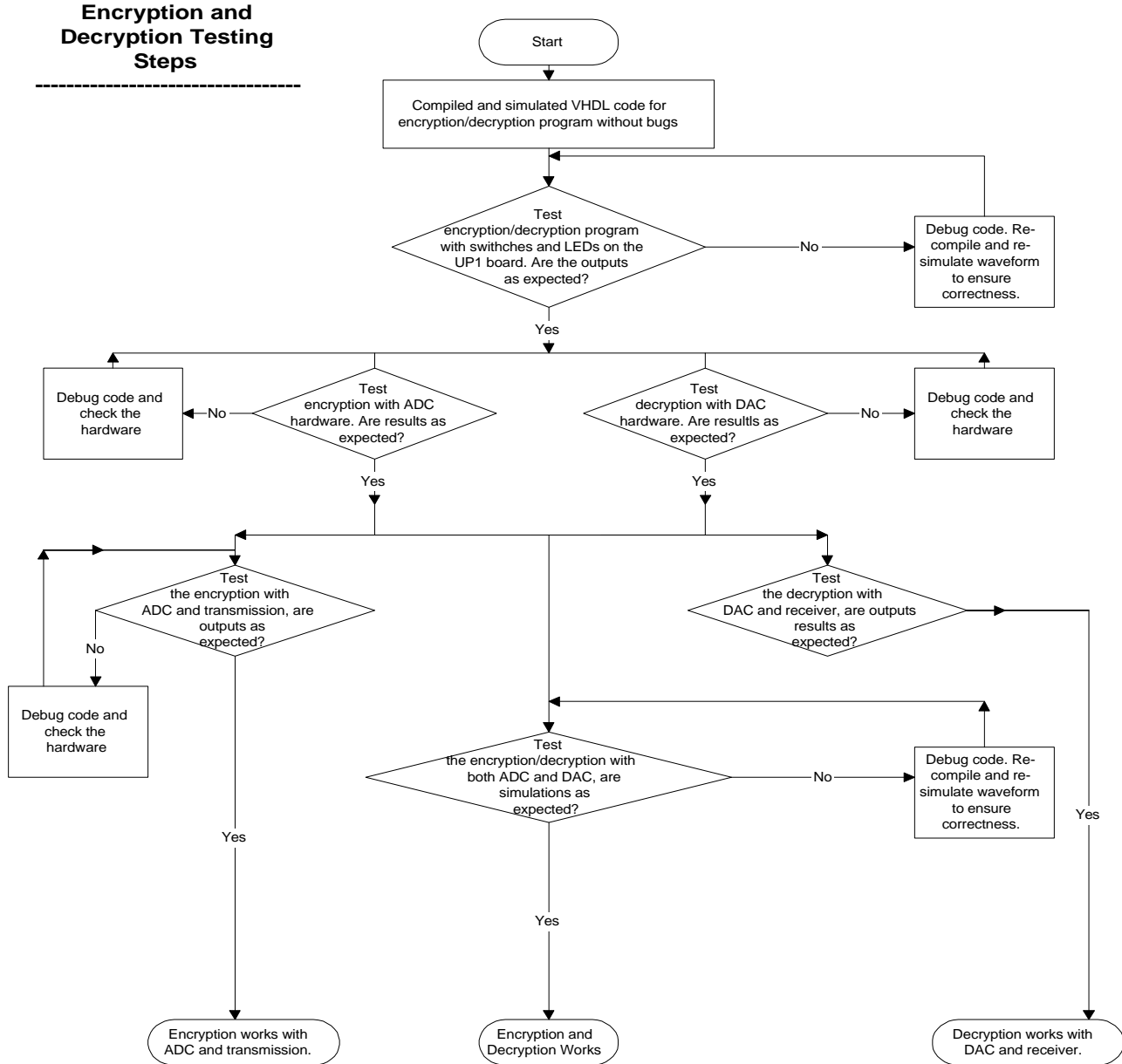11.2 Encryption/Decryption

The flowchart below describes the sequential testing cases for the encryption/decryption algorithm:



All three LFSRs are tested in the same manner. Each LFSR is seeded with a hard-coded key, the enable line is always high, and a clock with a 20.0ns period is used. After every clock cycle, the LFSR outputs one bit. The value of this bit, as well as the value stored in the register, is compared with the results obtained by hand. These comparisons are summarized in the tables below.

Table 11.2.1: LFSR-8 Test Results

Correct LFSR Value (Binary)	LFSR Value from Simulation (Bin)	LFSR Value on Waveform (Hex)	Correct LFSR Output (Binary)	LFSR Output from Simulation (Bin)
00001000	00001000	08		
10000100	10000100	84	0	0
01000010	01000010	42	0	0
10100001	10100001	A1	0	0
11010000	11010000	D0	1	1
11101000	11101000	E8	0	0
01110100	01110100	74	0	0
10111010	10111010	BA	0	0
11011101	11011101	DD	0	0
11101110	11101110	EE	1	1
01110111	01110111	77	0	0
00111011	00111011	3B	1	1
00011101	00011101	1D	1	1
00001110	00001110	0E	1	1
10000111	10000111	87	0	0
11000011	11000011	C3	1	1
01100001	01100001	61	1	1
00110000	00110000	30	1	1
00011000	00011000	18	0	0

Note: XORing bits 8, 4, 3, and 2 in the LFSR obtain the output bit.

Table 11.2.2: LFSR-11 Test Results

Correct LFSR Value (Binary)	LFSR Value from Simulation (Bin)	LFSR Value on Waveform (Hex)	Correct LFSR Output (Binary)	LFSR Output from Simulation (Bin)
00000001011	00000001011	00B		
10000000101	10000000101	405	1	1
11000000010	11000000010	602	1	1
01100000001	01100000001	301	0	0
00110000000	00110000000	180	1	1
00011000000	00011000000	0C0	0	0
00001100000	00001100000	060	0	0
00000110000	00000110000	030	0	0
00000011000	00000011000	018	0	0
00000001100	00000001100	00C	0	0
00000000110	00000000110	006	0	0
10000000011	10000000011	403	0	0
01000000001	01000000001	201	1	1
00100000000	00100000000	100	1	1
00010000000	00010000000	080	0	0
00001000000	00001000000	040	0	0
00000100000	00000100000	020	0	0
00000010000	00000010000	010	0	0
00000001000	00000001000	008	0	0

Note: XORing bits 11 and 2 in the LFSR obtain the output bit.

Table 11.2.3: LFSR-13 Test Results

Correct LFSR Value (Binary)	LFSR Value from Simulation (Bin)	LFSR Value on Waveform (Hex)	Correct LFSR Output (Binary)	LFSR Output from Simulation (Bin)
0000000001101	0000000001101	000D		
1000000000110	1000000000110	1006	1	1
0100000000011	0100000000011	0803	0	0
1010000000001	1010000000001	1401	1	1
0101000000000	0101000000000	0A00	1	1
0010100000000	0010100000000	0500	0	0
0001010000000	0001010000000	0280	0	0
0000101000000	0000101000000	0140	0	0
0000010100000	0000010100000	00A0	0	0
0000001010000	0000001010000	0050	0	0
0000000101000	0000000101000	0028	0	0
1000000010100	1000000010100	1014	0	0
0100000001010	0100000001010	080A	0	0
1010000000101	1010000000101	1405	0	0
1101000000010	1101000000010	1A02	1	1
1110100000001	1110100000001	1D01	0	0
0111010000000	0111010000000	0E80	1	1
0011101000000	0011101000000	0740	0	0
0001110100000	0001110100000	03A0	0	0

Note: XORing bits 13, 4, 3, and 1 in the LFSR obtains the output bit.

The keystream generator entity contains four components:

1. an 8-bit maximal length linear feedback shift register
2. a 11-bit maximal length linear feedback shift register
3. a 13-bit maximal length linear feedback shift register
4. a 2-to-1 multiplexer

The 8-bit LFSR output and the 11-bit LFSR output are used as the inputs to the multiplexer. The output of the 13-bit LFSR feeds into the multiplexer select line. During simulation of this entity, the enable line is always high and the clock has a period of 20.0ns. After every clock cycle, the keystream generator outputs one bit. The value of this bit is compared with the results obtained by hand as shown in the table below.

Table 11.2.4: Keystream Generator Test Results

Correct Generator Output Bit (Binary)	Generator Output Bit from Simulation (Binary)
0	0
1	1
0	0
1	1
0	0
0	0
0	0
0	0
0	0
0	0
0	0
0	0
1	1
1	1
0	0
0	0
1	1
0	0
0	0

The stream cipher entity contains two components:

1. a 1-bit 2-input register
2. the key generator

Plaintext bits feed serially into one input of the register, and the keystream feeds serially into the other register input. The register latches 1 bit from each input at the rising edge of every clock cycle. Then the two bits are XORed to produce a ciphertext bit.

This entity compiles and simulates correctly. The test cases used are the following:

1. plaintext stream of all 0's
2. plaintext stream of all 1's
3. plaintext stream pattern of 101010...

The results of these tests are summarized in the tables below.

Table 11.2.5: Plaintext Stream of All 0's Test Case

Plaintext Bit (Binary)	Keystream Bit (Binary)	Correct Ciphertext (Binary)	Ciphertext from Simulation (Binary)
0	0	0	0
0	1	1	1
0	0	0	0
0	1	1	1
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	1	1	1
0	1	1	1
0	0	0	0
0	0	0	0
0	1	1	1
0	0	0	0
0	0	0	0

Table 11.2.6: Plaintext Stream of All 1's Test Case

Plaintext Bit (Binary)	Keystream Bit (Binary)	Correct Ciphertext (Binary)	Ciphertext from Simulation (Binary)
1	0	1	1
1	1	0	0
1	0	1	1
1	1	0	0
1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1
1	1	0	0
1	1	0	0
1	0	1	1
1	0	1	1
1	1	0	0
1	0	1	1
1	0	1	1

Table 11.2.7: Plaintext Stream Pattern of 1010... Test Case

Plaintext Bit (Binary)	Keystream Bit (Binary)	Correct Ciphertext (Binary)	Ciphertext from Simulation (Binary)
1	0	1	1
0	1	1	1
1	0	1	1
0	1	1	1
1	0	1	1
0	0	0	0
1	0	1	1
0	0	0	0
1	0	1	1
0	0	0	0
1	0	1	1
0	1	1	1
1	1	0	0
0	0	0	0
1	0	1	1
0	1	1	1
1	0	1	1
0	0	0	0

The complete stream cipher contains a serial-to-parallel converter. The input data is fed serially. The output is the encrypted data, but it is sent 8 bits in parallel. The valid_in line is held high for 8 clock cycles indicating the inputs during that time are valid data. The output is not considered valid (and therefore, not read) until the valid_out line is high.

Table 11.2.8: Plaintext Stream of All 0's Test Case

Plaintext Bit (Binary)	Correct Ciphertext in Serial (Binary)	Valid_out	Ciphertext from Simulation (Binary)
0	0	0	00000000
0	1	0	00000000
0	0	0	00000000
0	1	0	00000000
0	0	0	00000000
0	0	0	00000000
0	0	0	00000000
0	0	0	00000000
0	0	0	00000000
0	0	1	00001010
0	0	0	00000000
0	0	0	00000000
0	0	0	00000000
0	1	0	00000000
0	1	0	00000000
0	0	0	00000000
0	0	0	00000000
0	1	0	00000000
0	0	1	10011000

Table 11.2.9: Plaintext Stream of All 1's Test Case

Plaintext Bit (Binary)	Correct Ciphertext in Serial (Binary)	Valid_out	Ciphertext from Simulation (Binary)
1	1	0	00000000
1	0	0	00000000
1	1	0	00000000
1	0	0	00000000
1	1	0	00000000
1	1	0	00000000
1	1	0	00000000
1	1	0	00000000
1	1	0	00000000
1	1	1	11110101
1	1	0	00000000
1	1	0	00000000
1	1	0	00000000
1	0	0	00000000
1	0	0	00000000
1	1	0	00000000
1	1	0	00000000
1	0	0	00000000
1	0	1	01100111

Table 11.2.10: Plaintext Random Stream Test Case

Plaintext Bit (Binary)	Correct Ciphertext in Serial (Binary)	Valid_out	Ciphertext from Simulation (Binary)
1	1	0	00000000
0	1	0	00000000
1	1	0	00000000
0	1	0	00000000
1	1	0	00000000
0	0	0	00000000
1	1	0	00000000
0	0	0	00000000
		1	01011111
0	0	0	00000000
1	1	0	00000000
1	1	0	00000000
0	1	0	00000000
0	1	0	00000000
1	1	0	00000000
0	0	0	00000000
1	0	0	00000000
		1	00111110

To test the decryption/DAC compound entity, the input pins are connected to switches and the output of the DAC is observed using an oscilloscope. The input (set by the switches) is treated as encrypted data, and is fed into the decryptor. After decryption, the output is fed into the DAC to be converted to analog. Since the input is constant, the output should be constant as well.

Two 8-bit signals are input consecutively to ensure that the decryption entity is producing the correct key stream. To indicate when the data is valid, a push button is used. After inputting two 8-bit binary numbers, the system is reset (using another push button). This returns the LFSRs to their initial state.

The table below summarizes the results of the testing. The input is set using the switches where a switch that is “on” refers to a logic “1.” The output is the data that should output from the decryption entity and is not explicitly checked during the test. The measured voltage is the output from the DAC and is observed on the oscilloscope. The calculated voltage is the theoretic voltage value of the DAC output, which is determined from the equation $V_o = 10V(A_1/2 + A_2/4 + \dots + A_8/256)$ where A1-A8 are the inputs to the DAC, i.e. decrypted data.

Table 11.2.11: Decryption/DAC Integration Test Results

Input – Encrypted Data (Binary)	Output -- Decrypted Data (Binary)	Measured Voltage (V)	Calculated Voltage (V)
11110101	11111111	10.20	9.96
10101011	00110011	2.00	1.99
10100000	10101010	6.80	6.64
00000011	10011011	6.20	6.05
00001010	00000000	0.00	0.00
11011000	01000000	2.84	2.50

To test the ADC/Encryption compound entity, a function generator is connected to the input pins and the output pins are connected to the DAC. The input waveform before the ADC and the output waveform after the DAC are observed and compared using the oscilloscope. The outputs of the encryption entity are also observed on the oscilloscope.


Each output waveform from the 8 parallel bits of the encryption entity is a non-periodic square-waveform. This represents the logic 0s and 1s of the encrypted data. However, the rate at which this data is output is much too fast to check or display on LEDs. The minimum speed at which the ADC can properly operate is still too fast for the human eye to see. Thus, the outputs of the encryptor are fed into the DAC.

The output of the DAC is then compared to the input waveform. The output is an irregular, non-periodic waveform. It does not resemble the input waveform, as expected. The output of the encryptor should be noise, as confirmed.

11.3 Transmission/Receive

The flowchart below describes the sequential testing cases for the transmission/receive algorithm:

Transmission Design Testing Steps

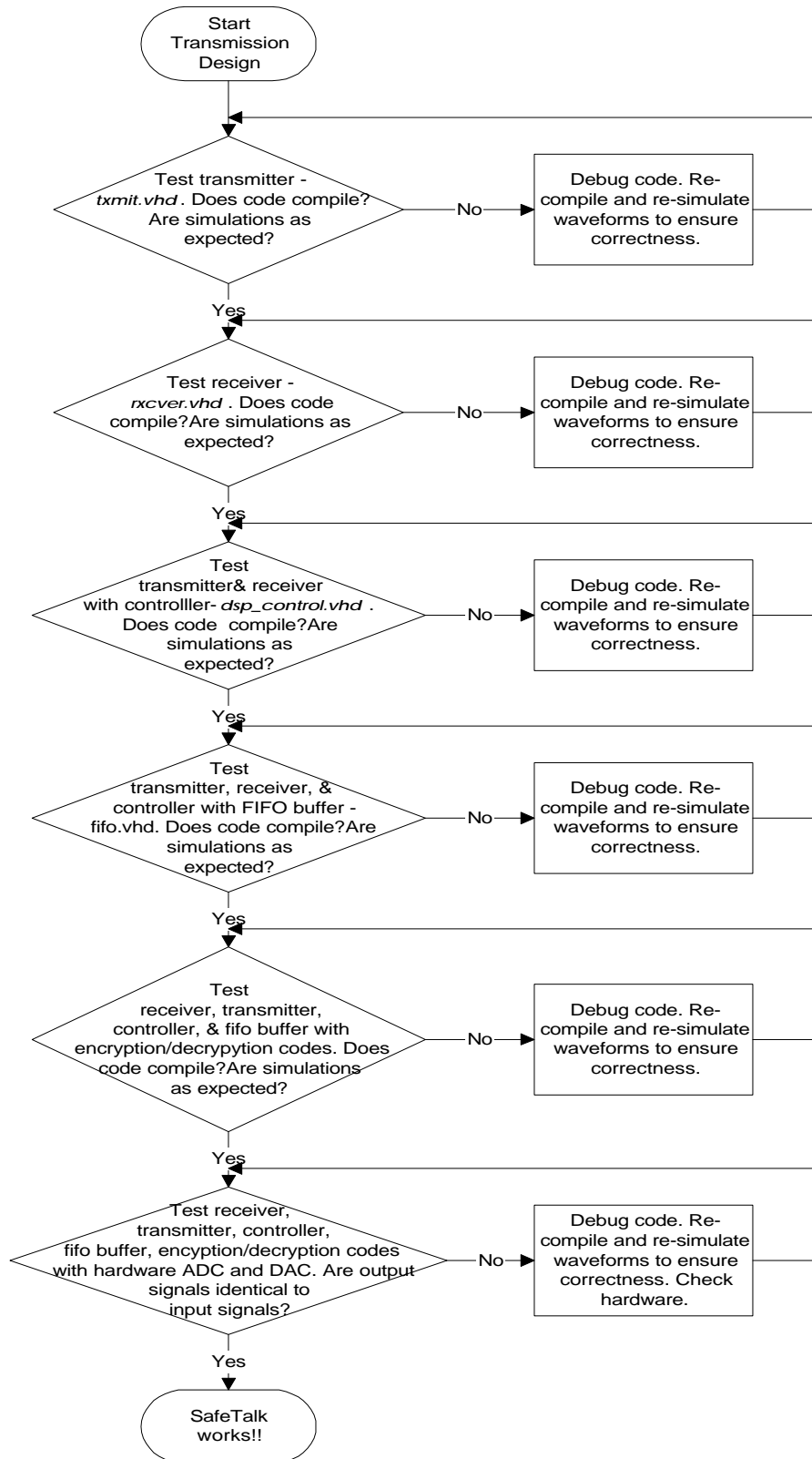

Test Case 11.3.1

Transmit module testing (*txmit.vhd*)

The testing of the transmitter was done by sending the transmitter the required signals and data. Once the parallel input data of the transmitter module is sent out of the serial line, the two values can be compared for validation. During the testing of the transmit module the baud rate clock was set to divide the master clock by 4. This was done to reduce the size/length of the output waveform, thereby simplifying the verification of the waveform.

The 8-bit data bus was latched to four different values so that the outputs on the serial transmit line could be validated. The values used in the tests were EF, A5, 55 and 00.

Table 11.3.1: Parallel Input vs. Serial Output

Parallel input	Expected serial output			
	Start bit	8 data bits	Parity bit (even)	Stop bit
EF	0	11110111	1	1
A5	0	10100101	0	1
55	0	10101010	0	1
00	0	00000000	0	1

Note: the 8 data bits are transmitted with LSB first.

Test Case 11.3.2

Receive module testing (*rxcvr.vhd*)

The testing of the receiver module was similar to the testing of the transmitter module. The receiver module now functions correctly. It can be seen, from the waveform, that the data was read in correctly from the serial input and correctly latched to the *receive* hold register.

Table 11.3.2: Serial Input vs. Parallel Output

Expected serial input				Parallel output
Start bit	8 data bits	Parity bit (even)	Stop bit	
0	11110111	1	1	EF
0	10100101	0	1	A5
0	10101010	0	1	55
0	00000000	0	1	00

Note: the 8 data bits are received with LSB first.

The data chosen, for the testing of the transmitter and receiver modules, contain 1's and 0's in varying orders thereby testing to ensure that the respective modules can interpret the received/transmitted serial signal.

Test Case 11.3.3

DSP module testing (*dsp_ctrl.vhd*)

The testing of the DSP control transmitter was done by giving it parallel input of 6 different values. The serial output obtained were then compared to the parallel input values to ensure proper transmission has taken place.

Table 11.3.3: Parallel Input vs. Serial Output 2

Parallel input	Expected serial output			
	Start bit	8 data bits	Parity bit (even)	Stop bit
11	0	10001000	0	1
22	0	01000100	0	1
55	0	10101010	0	1
00	0	00000000	0	1
A5	0	10100101	0	1
33	0	11001100	0	1

Note: the 8 data bits are transmitted with LSB first.

The testing of the DSP receiver control was similar but with the input as serial and the output as parallel. The inputs were compared to the outputs to determine the validity of the reception.

Table 11.3.4: Serial Input vs. Parallel Output 2

Serial input				Expected Parallel output
Start bit	8 data bits	Parity bit (even)	Stop bit	
0	10001000	0	1	11
0	01000100	0	1	22
0	10101010	0	1	55
0	00000000	0	1	00
0	10100101	0	1	A5
0	11001100	0	1	33

Note: the 8 data bits are received with LSB first.

Note that the above DSP module tested contains the UART and FIFO buffers.

11.4 DAC

Test Case 1:

In order to test the D/A converter, a simple VHDL code was used to assign the digital inputs to the DAC0806 chip. Please refer to the VHDL code called *dac.vhd* in the **Appendix**. The *dac.vhd* is a program that provides an 8-bit digital input to the DAC by switching the eight switch buttons. The code was programmed on the EPF10K20 device of the UP1 Education Board. The FLEX_SW1 switches were used to provide logic-level signals to eight-output pin on the EPF10K20 device.

Table 11.4.1 : FLEX_EXPAN_A Signal Names & Device connections

Hole Number On the up1 board	Pin number for the DAC0806
15	12(LSB)
16	11
17	10
18	9
19	8
20	7
21	6
22	5 (MSB)

The above hole number was connected to the input pins of the DAC0806 chips according to the pin label of the chips. Each switch represented different input bit. Therefore, when all the switches were on, the digital input of the DAC would be 11111111. The result voltage V_{out} from the LF351 would be equal to $V_{out} = 10V(1/2 + 1/4 + 1/8 + 1/16 + 1/32 + 1/64 + 1/128 + 1/256) = 9.96V$ according to the formula that given from the datasheet of the chips.

$$V_{out} = V_{ref}(A1/2 + A2/4 + A3/8 + A4/16 + A5/32 + A6/64 + A7/128 + A8/256),$$

where $V_{ref}=10V$, A1 to A8 represent the 8 digital inputs

Table 11.4.2: Test cases, test results and the calculated results.

The switches that were OFF	Digital input	TEST RESULT (measured values of V_{out})	Calculated values of $V_{out}(V)$
None(all ON)	11111111	9.98 V	9.96
S8 (Switch-8)	11111110	9.68 V	9.92
S7, S8	11111100	9.52 V	9.84
S6, S7, S8	11111000	9.44 V	9.68
S5, S6, S7, S8	11110000	9.40 V	9.37
S4, S5, S6, S7, S8	11100000	8.77 V	8.75
S3, S4, S5, S6, S7, S8	11000000	7.52 V	7.50
S2, S3, S4, S5, S6, S7, S8	10000000	5.91 V	5.00
All	00000000	0.002 V	0.00

The measured voltage values from the test were very close to the calculated values. This showed that the DAC part worked properly with the switch inputs.

Test Case 2:

The second test of the complete design of the Digital-to-Analog converter (DAC) is done by input the digital inputs by an 8-bits counter. The counter is constructed by the VHDL code, and the program is called **dsctest.vhd**. This program provides an 8-bits counter, which produces 8-bits binary number input to the DAC. The counter counts up from 0 to 255 and then counts down from 255 back to 0. The output of the counter is an 8 bits binary number, which will go to the 8-bits input of the DAC. The final output that produces from the DAC is an analog signal. The result of the analog signal is a triangular waveform by inputting the counter digital input. The triangular waveform is shown on the oscilloscope in the demonstration and is plotted below:

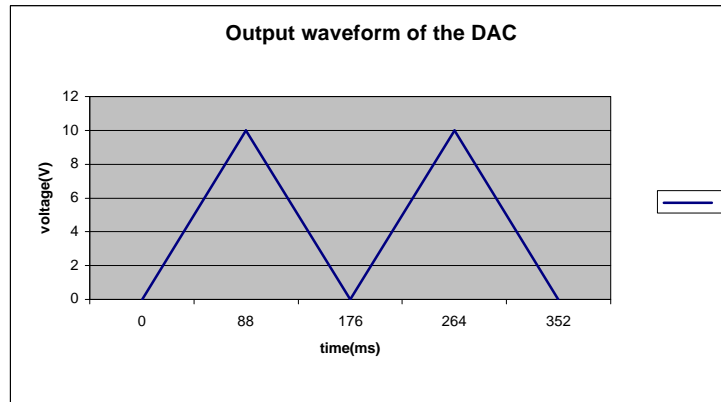


Figure 11.4.1 : Output from DAC

The signal produced from the DAC shows that as the counter counts up from zero to 255, the corresponding voltage increase from 0 to about 10V. The output voltage drops when the counter reaches 255 and then starts to count down. A clock divider is used in the counter program to control the input time, the input comes into the DAC with frequency = $25.175\text{MHz} / 10000 = 2517.2\text{Hz}$. This frequency can be change by changing the clock divider value.

After the connection of the low-pass filter, the output analog signal from the filter becomes a smooth signal. The signal is sketched from the oscilloscope and is shown in the following diagram.

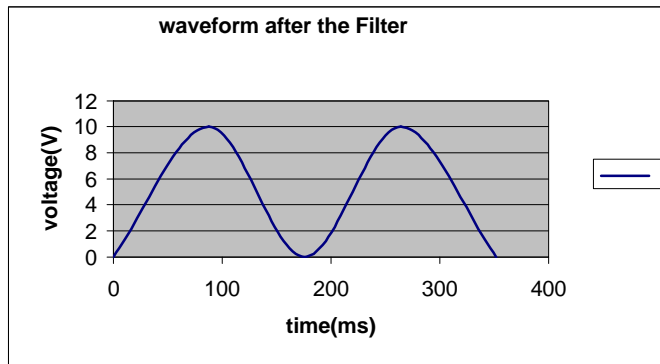


Figure 11.4.2: Filter Output

Test Case 3:

Combining the A/D to the D/A, we used the function generator as an input waveform going into the A/D. The outputs produced by the D/A circuit are exactly similar to that of the input waveform produced by the function generator. The clock frequency used was approximately 840kHz. This is due to the design limitations of the DAC circuit. Listed below are some of the test cases done using the function generator:

Input waveform was a sinusoidal wave.

	Frequency of the Input Waveform (Hz)	Input Voltage into ADC ($V_{\text{peak-to-peak}}$)	Period of Waveform into ADC		Output Voltage received at DAC ($V_{\text{peak-to-peak}}$)	Period of Waveform from DAC		Time delay of the output from DAC (phase shift between the input and output)
			(Hz)	(ms)		(Hz)	(ms)	
1	10	1	10	100	4.76	10	100	384.6Hz(2.6ms)
2	100	1	100	10	2.88	100	10	90.91Hz(11ms)
3	1000	1	1000	1	1.02	1000	1	2kHz(500us)

The plots below illustrate the waveforms observed from the oscilloscope:

Trial 1:

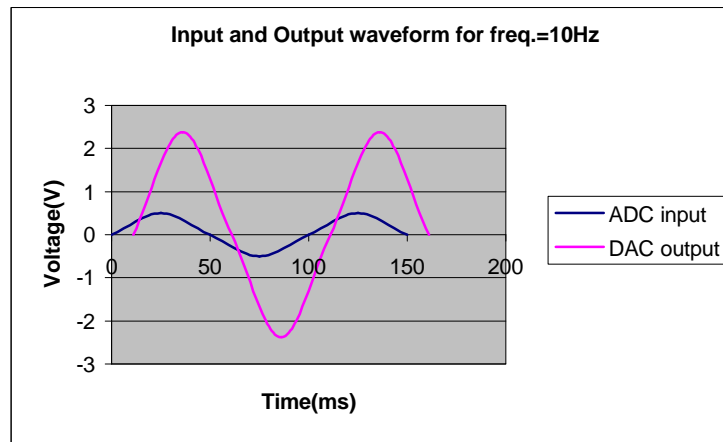


Figure 11.4.3

Trial 2:

 


Figure 11.4.4

Trial 3:

 


Figure 11.4.5

Note : These graphs are plotted using Microsoft Excel and the waveforms (lines) produced are very much more fine than the ones observed on the oscilloscope. Due to noise interference and other disturbances that occurred with the input signal, the sinusoidal waveform seen on the oscilloscope is courser and 'dirtier' than the ones plotted using Excel.

The amplitudes of the input signal for the test cases 1 are fixed to be equal to 1V_{peak-to-peak}. The input and output waves are tested by probing the signals with the oscilloscope probe. The amplitude of the output voltage is greater than the input wave due to the fact of the amplifier. The waveform shows that the frequency of the output waveform is the same as the input wave. However, there is a phase shift between the input and output signal, due to the propagation delay. From observation of the results, the delay increases with the input signal frequency. Test cases was performed up to 1000Hz due to limitations of the ADC circuit. All of the input signals with frequency greater than 3KHz will cutoff since the low-pass filter in the DAC and ADC was designed to have a cut-off frequency of 3000Hz (bandwidth used in telephone communications).

12. VHDL Source Code Index

- ◆ clock_divider.vhd
- ◆ input_reader.vhd
- ◆ comp.vhd
- ◆ p_out_stream_cipher_pkg.vhd
- ◆ p_out_stream_cipher.vhd
- ◆ s_to_p_data_conv.vhd
- ◆ txmit.vhd
- ◆ rxcvr.vhd
- ◆ fifo.vhd
- ◆ dsp_ctrl_pkg.vhd
- ◆ dsp_ctrl.vhd
- ◆ dsctest.vhd
- ◆ dac.vhd

13. Test Bench Index

- ◆ clock_divider_test.vhd
- ◆ comp_test.vhd
- ◆ dsp_testbench.vhd
- ◆ dac_test.vhd

A. Appendix : Data Sheets

SafeTalk

SafeTalk prototype v1.0
Secure Telecommunications Module

General Description:

SafeTalk is used for secure telecommunication where privacy is desired.

Features:

- Secure telecommunication with a companion (v1.0 has basic encryption. Later implementations will incorporate stronger encryption)
- Asynchronous data transmission using a UART.

Key Specifications:

- 8-bit linear ADC
- 8-bit linear DAC
- Stream cipher encryption/decryption
- Asynchronous data transmission using a UART

Functional Description:

SafeTalk uses an 8-bit linear ADC and DAC for conversion between analog and digital. The digital signal processing performed includes encryption and decryption of the digital samples. With version 1.0 no compression or decompression has been implemented. As a result the data rate required for transmission is higher than it should be. At a sampling rate of 8000 kHz, the data rate required is about 88 kbps. The modem that we would use with SafeTalk would have a data rate of 33.6 kbps. With compression this data rate would be achievable.

Logic blocks required: 884