

Nov 29, 2001



Electrical & Computer Engineering

EE552
High Level
Digital ASIC
Design using
CAD

C-RAM Parallel Computer

Presented By

Shahid Aslam Khan

Sue Ann Ung

Satneev Bhamra

About this Project


- Computational RAM (C-RAM)
- In a nutshell:
 - C-RAM
 - Memory
 - Processing Elements (PE)
 - Single Instruction Multiple Data architecture (SIMD)
 - Parallel Computation
 - Applications:
 - Signal and Image Processing
 - Computer Graphics
 - Database, etc.

Outline

- The C-RAM Computer
- The C-RAM Parallel Processor System
- The Sequencer
- The Controller
- C-RAM Architecture
- PE Model
- IO Interface
- Chip Overview
- Achievements
- Acknowledgements
- Demo


The C-RAM Computer

 - Broken down into 4 components
 - control unit
 - processing elements
 - memory modules
 - IO interfaces




The C-RAM Parallel Processor System

 - Controller
- Counter/Sequencer
- RAM
- IO




The Sequencer

- Minimalist Microcoded Sequencer

 


- Opcodes and Memory instructions

 


The Controller

 - Based on a simple decoder
- Case statement in VHDL code
- Selects address
 - to read from the RAM or
 - to write to the RAM
- Issues opcodes or instructions to the PE




CRAM Architecture

 - Implemented using SRAM cells on the Altera Board
- SIMD instructions come from the sequencer in the main controller
- Opcodes are routed to the individual PEs




PE Model

 - X and Y, 1 bit registers
- ALU
- 8 bit global instruction
- Data shifting
- Conditional Operations



IO Interface

 - Internal ROM / RAM for opcodes and instruction
- 2-line LCD
- 2 Seven Segment Display



Chip Overview

Module	Logic Cells required
PE (1)	12 (1 %)
PE (2)	36 (3 %)
Controller	78 (6%)
I/O	254 (22%)
Total*	344 (30 %)

PE*: only one PE

- **Memory**
 - **256 x 16-bit instruction ROM initialized by .mif file**
 - **256 x 1-bit data RAM initialized by .mif file**
- **IO**
 - **7 segment display to show results of PE elements and memory**
 - **LCD display to show instruction set in the ROM**
- **Performance of C-RAM = 22.17 MHz**
- **Uses only 30% (with 1 PE) of the Altera FLEX10K20 Logic Cells**

Achievements

- What the system can do now
 - More than one PE modules
 - Read and Write from/to the RAM
 - Logical Functions – Negation, OR, AND etc
 - Addition, Subtraction, Copy etc
- Improvements that needed to be made
 - Add more operations such as multiplication and division
 - Use ARM processor as a host to C-RAM module

Acknowledgements

- Elliott, Duncan G., Stumm, Michael, Snelgrove, W. Martin, Cojocaru, Christian, McKenzie, Robert (1999). *Computational RAM: Implementing Processors in Memory* (p32-41) IEEE Design and Test of Computers January – March 1999
- Elliott, Duncan G. (1998). *Computational RAM: A Memory – SIMD Hybrid*
Phd Thesis, The University of Toronto
- Akllilu, Noah, Elliott, Duncan G., Wickman, Curtis A. *A Tightly Coupled Hybrid SIMD/SISD System.*
MSc Thesis, The University of Alberta

Demo

Addition Algorithm on C-RAM

Elliott, Duncan G. (1998). *Computational RAM: A Memory – SIMD Hybrid*
Phd Thesis, The University of Toronto

```
select B[least_significant_bit]
    X = M          // first bit is a special case with
                    no carry in
select A[least_significant_bit]
    Y = M&X        // Calculate carry
    M = X = X^M    // Calculate sum and write
                    back
for j = least significant bit + 1..most significant bit
    select B[j]
        X = M^Y   // sum B[j] and carry in
        Y = M&Y   // carry out
    select A[j]
        Y = Y | (M&X) // carry out
        M = X = X^M    // sum A[j] and partial
                        sum, write back
end for
```

Instructions

0000000000000000; ---Address of B(0)

1101010100000010; --- X = M

1101010100000000; -- disable x

0000000000000010; ---Address of A(0)

1101000000000100; -- Y = M&X

1010110100000000; -- opcode to get X^M

1010110100001000; -- M = X^M enabling
memory

1010110100000010; -- X = X^M enabling x
register

0000000000000001; -- Address of B(1)

1011001100000010; -- X = M^Y

1100010000000100; -- Y = M&Y

00000000000000101; -- Address of A(1)

1111011000000100; -- Y = $Y|(M&X)$

0101101000000000; -- opcode to get X^M

1010110100001000; -- M = X^M enabling
memory

1010110100000010; -- X = X^M enabling x
register

1010110100000000; -- disable x

0000000000000010; -- Address of B(2)

00000000 : 1; --Data in B(0)

00000100 : 1; --Data in A(0)

00000001 : 1; --Data in B(1)

00000101 : 1; --Data in A(1)

00000110 : 1; --Data in A(2)

00000010 : 0; --Data in B(2)