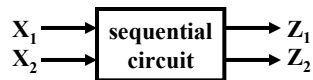


## Lecture 30. Multiple Inputs and Outputs


### Multiple Inputs and Outputs

A given sequential circuit may have multiple inputs and outputs

- e.g. two inputs  $X_1$  and  $X_2$ , and two outputs  $Z_1$  and  $Z_2$



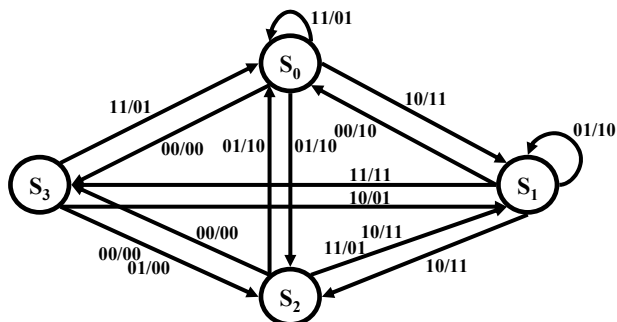
- the circuit is described by the following state machine


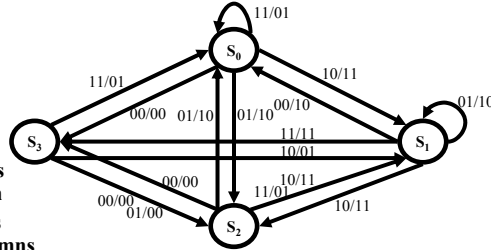
## Multiple Inputs and Outputs

A given sequential circuit may have multiple inputs and outputs

- e.g. two inputs  $X_1$  and  $X_2$  and two outputs  $Z_1$  and  $Z_2$



- state table
  - in case of Moore machine it has single "present output" column
  - in case of Mealy machine it has multiple "present output" columns

present state	next state				present output $Z_1Z_2$			
	$X_0X_1=00$	$X_0X_1=01$	$X_0X_1=10$	$X_0X_1=11$	$X_0X_1=00$	$X_0X_1=01$	$X_0X_1=10$	$X_0X_1=11$
$S_0$	$S_3$	$S_2$	$S_1$	$S_0$	00	10	11	01
$S_1$	$S_0$	$S_1$	$S_2$	$S_3$	10	10	11	11
$S_2$	$S_3$	$S_0$	$S_1$	$S_1$	00	10	11	01
$S_3$	$S_2$	$S_2$	$S_1$	$S_0$	00	00	01	01

## Multiple Inputs and Outputs

A given sequential circuit may have multiple inputs and outputs

- the state table can be simplified by use single (decimal) inputs and outputs

present state	next state				present output $Z_1Z_2$			
	$X_0X_1=00$	$X_0X_1=01$	$X_0X_1=10$	$X_0X_1=11$	$X_0X_1=00$	$X_0X_1=01$	$X_0X_1=10$	$X_0X_1=11$
$S_0$	$S_3$	$S_2$	$S_1$	$S_0$	00	10	11	01
$S_1$	$S_0$	$S_1$	$S_2$	$S_3$	10	10	11	11
$S_2$	$S_3$	$S_0$	$S_1$	$S_1$	00	10	11	01
$S_3$	$S_2$	$S_2$	$S_1$	$S_0$	00	00	01	01


present state	next state				present output $Z_1Z_2$			
	$X=0$	$X=1$	$X=2$	$X=3$	$X=0$	$X=1$	$X=2$	$X=3$
$S_0$	$S_3$	$S_2$	$S_1$	$S_0$	0	2	3	1
$S_1$	$S_0$	$S_1$	$S_2$	$S_3$	2	2	3	3
$S_2$	$S_3$	$S_0$	$S_1$	$S_1$	0	2	3	1
$S_3$	$S_2$	$S_2$	$S_1$	$S_0$	0	0	1	1

## Multiple Inputs and Outputs

A given sequential circuit may have multiple inputs and outputs

- the state table can be simplified by use single (decimal) inputs and outputs

present state	next state				present output $Z_1 Z_2$			
	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
$S_0$	$S_3$	$S_2$	$S_1$	$S_0$	0	2	3	1
$S_1$	$S_0$	$S_1$	$S_2$	$S_3$	2	2	3	3
$S_2$	$S_3$	$S_0$	$S_1$	$S_1$	0	2	3	1
$S_3$	$S_2$	$S_2$	$S_1$	$S_0$	0	0	1	1

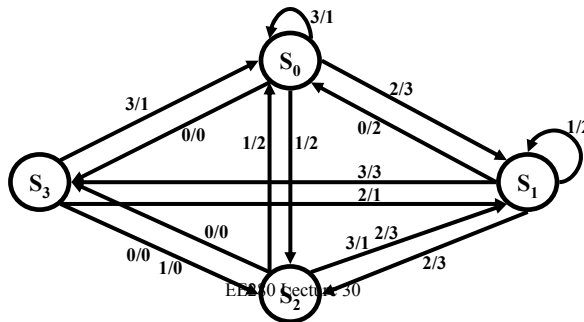


30 - 5
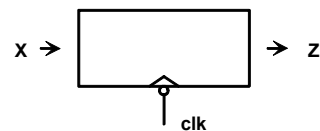
## Design Example

Derivation of state tables

- we will design a single input (X) / single output (Z) sequential circuit



- consider design of a sequence detector

- design network so that any input sequence ending in 101 will produce an output  $Z = 1$  coincides with the last input  $X = 1$ .
- network does not reset

e.g.: Typical I/P and corresponding O/P:

X = 0 0 1 0 1 0 0 1 1 1 0 1 0 0 1


Z =

## Design Example
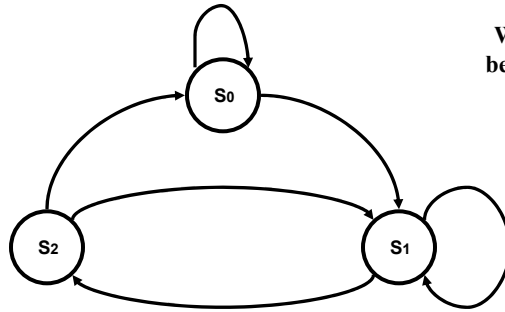
### Derivation of state tables for the sequence detector

- the considered circuit assumes Mealy network representation
  - first we construct a state graph to show the sequence of states and outputs in response to different inputs
  - start the network in a reset state  $S_0$
  - complete for all possible inputs

$x = 0\ 0\ 1\ 0\ 1\ 0\ 0\ 1\ 1\ 1\ 0\ 1\ 0\ 0\ 1$   
 $z = 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0$




We need two outgoing edges because 'X' can assume 0 or 1

## Design Example
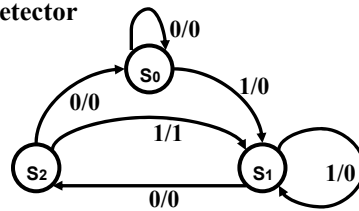
### Derivation of state tables for the sequence detector

- the considered circuit assumes Mealy network representation
  - next we convert the state graph to state table




Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
$S_0$	$S_0$	$S_1$	0	0
$S_1$	$S_2$	$S_1$	0	0
$S_2$	$S_0$	$S_1$	0	1

## Design Example
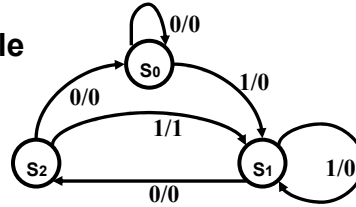
### Sequence detector

- the considered circuit assumes Mealy network representation
  - next we convert the state table to the transition table
  - since we have 3 states we need 2 FF's: A, B
    - 1 FF remembers 2 states: 0, 1
    - 2 FF's remember 4 states: 00, 01, 10, 11
    - 3 FF's remember 8 states: 000, 001, ..., 111



Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
S <sub>1</sub>	S <sub>2</sub>	S <sub>1</sub>	0	0
S <sub>2</sub>	S <sub>0</sub>	S <sub>1</sub>	0	1


A	B	Present Output	
		X = 0	X = 1
0	0	0	0
0	1	0	0
1	0	0	1

## Design Example

### Sequence detector

- the considered circuit assumes Mealy network representation

A	B	Present Output	
		X = 0	X = 1
0	0	00	01
0	1	10	01
1	0	00	01

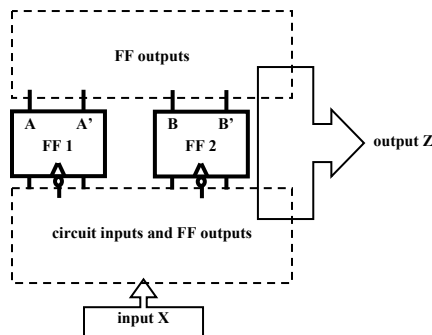

## Design Example

### Sequence detector

- the considered circuit assumes Mealy network representation
- next we construct "next state K-maps" for each FF and Z

A	B	A+ B+		Present Output	
		X = 0	X = 1	X = 0	X = 1
0	0	00	01	0	0
0	1	10	01	0	0
1	0	00	01	0	1

		X	
		0	1
AB	00	0	0
	01	1	0
	11	X	X
	10	0	0

A+

		X	
		0	1
AB	00	0	1
	01	0	1
	11	X	X
	10	0	1

B+


		X	
		0	1
AB	00	0	0
	01	0	0
	11	X	X
	10	0	1

Z+

## Design Example
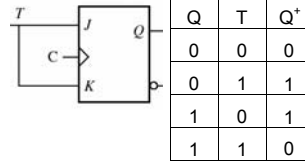
### Sequence detector

- the considered circuit assumes Mealy network representation
- A, B, and X are used to derive inputs to FFs
- we assume using T-FF and we design their input K-maps



		X	
		0	1
AB	00	0	0
	01	1	0
	11	X	X
	10	0	0

A+

		X	
		0	1
AB	00	0	0
	01	1	0
	11	X	X
	10	1	1

T<sub>A</sub>

		X	
		0	1
AB	00	0	1
	01	0	1
	11	X	X
	10	0	1

B+

		X	
		0	1
AB	00	0	1
	01	1	0
	11	X	X
	10	0	1

T<sub>B</sub>

## Design Example

### Sequence detector

- the considered circuit assumes Mealy network representation
- A, B, and X are used to derive inputs to FFs
- we assume using T-FF and we design their input K-maps

	X	0	1
AB		0	1
00		0	0
01		1	0
11		X	X
10		1	1

T<sub>A</sub>


	X	0	1
AB		0	1
00		0	1
01		1	0
11		X	X
10		0	1

T<sub>B</sub>

## Design Example
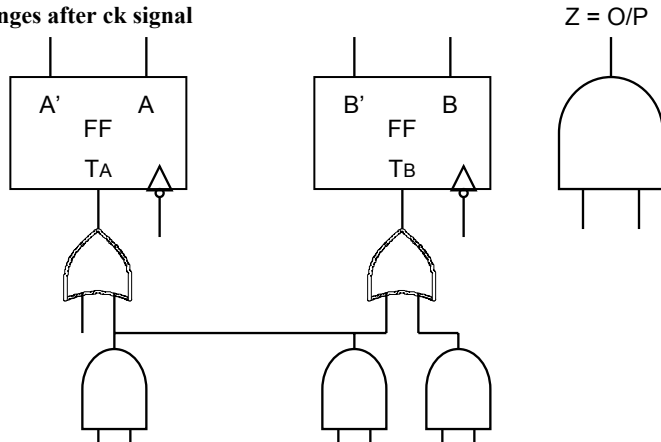
### Sequence detector

- the considered circuit assumes Mealy network representation
- FF state changes after ck signal



## Design Example

### Sequence detector - testing the design

- choose some inputs of interest, in this case let us consider:  $X = 1\ 1\ 0\ 1$
- look at the K maps for  $A+$ ,  $B+$ , and  $Z$  or follow the signals in the diagram

X	0	1
AB	00	01
00	0	0
01	1	0
11	X	X
10	0	0

$A+$

X	0	1
AB	00	01
00	0	1
01	0	1
11	X	X
10	0	1

$B+$

X	0	1
AB	00	01
00	0	0
01	0	0
11	X	X
10	0	1

$Z+$

A	B	X	Z	$A+$ $B+$
0	0	1	0	<input type="checkbox"/>
0	1	1	0	<input type="checkbox"/>
0	1	0	0	<input type="checkbox"/>
1	0	1	1	<input type="checkbox"/>

Remember...

