1 Objectives
2 Pre-Lab
2.1 Background
2.2 Equipment List
3 Procedure
3.1 Equipment Familiarization
3.1.1 Student PC Board
3.1.2 DC Power Supply
3.1.3 Digital Multimeter
3.1.4 Power Supply Cont
3.1.5 Decade Box
3.2 Ohms Law and Power Dissipation
3.3 Current Divider
3.4 Voltage Divider
3.5 Loading Effect
3.6 Clean-up
4 Post-Lab
4.1 Calculations
4.2 Graphs
4.3 Questions

ECE202 - Electrical Circuits I Electrical and Computer Engineering - University of Alberta

1 Objectives

The first lab session will have the students familiarize themselves with some common electrical tools and components used for circuits and use them to experimentally test and confirm the validity of concepts learned in the lectures. The objectives for this lab are therefore to:

- 1. Familiarize yourself with a common benchtop DC Power Supply and all of of its functions.
- 2. Familiarize yourself with the use of a Digital Multimeter to appropriately measure resistance, DC voltage and DC current.
- 3. Use the Resistors on the Student Printed Circuit Board to investigate Ohm's Law, Power Dissipated in a Resistor and Kirchoffs Laws.
- 4. Setup a circuit that demonstrates that a voltmeter can have a significant loading effect on a circuit.

These objectives should be kept in mind as the students work through the lab procedure.

2 Pre-Lab

Before attending the lab, please complete the following:

Note:

Labs are typically completed in groups of two, so please try to pair up before coming to the lab. Each student needs to complete the pre-lab and hand it in at the start of their scheduled lab session. Only one lab report is required to be handed-in per group which is due one week after the schedule lab session. If you can't find a partner we will either pair you up in the lab or you may also be permitted to work by yourself if there is an available station.

- 1. Completely read through the information discussed in the **Background** section below and please skim through this **lab manual** to become familiar with what will be required of you during the lab.
- 2. Familiarize yourself with the Equipment used in the first lab by going though the pages for each piece of equipment in the **Equipment List**.
- 3. Make sure you have either an electronic device with you where you can access this lab manual or print out the 🗳 Lab 1 Manual (./lab/lab1/ECE202-Lab1-Manual.pdf) before coming to your lab section.
- 4. Make sure you print out a 🗄 Lab 1 Results Sheet (./lab/lab1/ECE202-Lab1-results.pdf) to record all of your results. You only require one printout per group.
- 5. Complete the following on the **Lab 1 Results Sheet** before coming to the lab. Everything in light green on the results sheet is part of the prelab.
 - a. For the resistors in *table 1. RESISTORS A (4-band resistors)* and *table 2. RESISTORS B (5-band resistors)* determine the color code and tolerance for each resistor. Using the tolerance, calculate both the possible low value and high value that the actual resistance of that resistor should fall between.
 - b. For the *table 3. Series Resistors* and *table 4. Parallel Resistors* calculate the effective resistance of those two resistors when placed in the corresponding configuration.
 - c. For the *Current Divider* circuit in figure 10 calculate the total effective resistance that is seen by the supply for each setting of R_2 . Also calculate the supply current (I_S) and the currents through each branch I_{R1} and I_{R2} for each setting of R_2 .
 - d. For the *Voltage Divider* circuit in figure 12 calculate the total effective resistance that is seen by the supply for each setting of R_2 . Also calculate the supply current (I_S) and the voltages across each resistor V_{R1} and V_{R2} for each setting of R_2 .
 - e. For the *Loading Effect* circuit in figure 15 calculate the voltage drop across both R₁ and R₂ assuming no voltmeter is connected.
- 6. Complete these **Pre-lab Questions** on a seperate piece of paper to hand in at the beginning of your lab session. Make sure to include an appropriate title, your first and last name, CCID, student ID and your lab section at the top of the page.
 - a. The Digital Multimeter (DMM) used in the lab is the Fluke 175. This multimeter, like most have four input terminals on the front of the device. In your own words describe what each of these four input terminals are generally used for.
 - b. The DC Power Supply used in the lab is the BK Precision 1651A. This power supply has three independent supplies all in the same unit. List some of the features of each supply including its voltage and current ratings.
 - c. Resistors typically have two important ratings: its resistance and its wattage. All of the resistors on the Student Printed Circuit Board are rated at 1/4 Watt. Using a few example calculations explain how this wattage rating effects the amount of voltage that can be applied to different resistor values.

2.1 Background

- She Basics of DC Circuit Theory (https://www.electronics-tutorials.ws/dccircuits/dcp_1.html)
- Ohm's Law and Power (https://www.electronics-tutorials.ws/dccircuits/dcp_2.html)
- S Kirchoffs Circuit Laws (https://www.electronics-tutorials.ws/dccircuits/dcp_4.html)

- Solvage Divider (https://www.allaboutcircuits.com/textbook/direct-current/chpt-6/voltage-divider-circuits/)
- S Current Divider (https://www.allaboutcircuits.com/textbook/direct-current/chpt-6/current-divider-circuits/)
- S Resistors (https://www.allaboutcircuits.com/textbook/direct-current/chpt-2/resistors/)
- S Resistor Color Code (https://www.allaboutcircuits.com/tools/resistor-color-code-calculator/)
- Solve Voltage Sources (https://www.electronics-tutorials.ws/dccircuits/voltage-source.html)
- S Current Sources (https://www.electronics-tutorials.ws/dccircuits/current-source.html)
- Soltmeter Impact on Measured Circuit (https://www.allaboutcircuits.com/textbook/direct-current/chpt-8/voltmeter-impact-measured-circuit/)
- Ammeter Impact on Measured Circuit (https://www.allaboutcircuits.com/textbook/direct-current/chpt-8/ammeterimpact-measured-circuit/)

2.2 Equipment List

- Student Printed Circuit Board (equ-pcb.html)
- 🔗 BNC & Banana Cables (equ-cables.html)
- S DC Power Supply (equ-ps.html)
- **S** Digital Multimeter (equ-dmm.html)
- *S* Decade Box (equ-decade.html)

3 Procedure

3.1 Equipment Familiarization

3.1.1 Student PC Board



figure 1. Student Printed Circuit Board

- 1. Look at the Student Printed Circuit Board used for this lab and notice the different sections. Today we will only be using the sections labeled RESISTORS A and RESISTORS B.
 - a. **RESISTORS A** Is made up of 4-band 1/4 watt resistors of various values which are connected to a banana jacks on either end.
 - b. **RESISTORS B** Is made up of 5-band 1/4 watt resistors of various values which are connected to a banana jacks on either end but one side of all of the resistors is connected to a common point.
 - c. **RESISTORS C** Has 4 smaller resistance 5-band 1/4 watt resistors which are connected to a banana jacks on either end and typically used for current sensing.
 - d. **DIODE BRIDGE** Is made up of 4 rectifier diodes connected to banana jacks that are connected in a bridge configuration for the purpose of converting an AC voltage to a DC voltage. This is not used in this course.
 - e. **OP-AMP** Is an common operational amplifier which can be connected to banana plugs. This is also not used in this course.
 - f. **2m5H INDUCTOR** A 2.5mH inductor which can be connected to a banana plugs. It will be used in later in this course once you get into AC circuits.
 - g. **CAPACITORS** Is made up of 4 different capacitors connected to a banana jacks. they will also be used in later in this course once you get into AC circuits.

3.1.2 DC Power Supply



figure 2. BK Precision DC Power Supply (1651A)

Adjustable DC Voltage Source

2. Use the power supply as an adjustable DC voltage source and note the following features.

- a. Turn the power supply on using the power switch.
- b. Select the independant mode using the parallel/series/independant switch.
- c. Select channel A using the A/B switch to use the voltmeter and ammeter needle displays to monitor the voltage and current output for channel A.
- d. Both channel A and B have knobs to adjust the set-points for voltage and current. Make sure the current knob for channel A is not zero. Adjust the voltage knob for channel A and notice the needle movement on the voltmeter shows the output voltage for channel A.

Note:

If you adjust the current knob to zero notice that the voltage also goes to zero. When this happens you will also notice a red light come on above the output terminals.

e. Switch the A/B switch to channel B and notice that the voltage and current control knobs for channel B now operate in a similar fashion as channel A.

Note:

If the power supply is on all channels will always be active, the A/B switch only changes which channel is displayed on the volt and am-meters.

f. There is also a separate 5 volt fixed power supply that can supply up to 4 amps.

Adjustable DC Current Source

- 3. Use the power supply as an adjustable DC current source and note the following features.
 - a. Turn the power supply off and use a banana lead to short the red positive terminal to the black negative terminal of the channel A output terminals.
 - b. Select independant mode and channel A metering.
 - c. Turn the power supply back on.
 - d. Make sure the voltage knob for channel A is not zero. Adjust the current knob for channel A and notice the needle movement on the ammeter shows the output current for channel A.

Note:

The red light above channel A's output terminals is on when the power supply is in current control mode and off when the power supply is in voltage control mode. Therefore the current knob will only control the output current when the red light is on and the voltage knob will only control the output voltage when the red light is off. Which control mode is active will depend on which set-point the output reaches first: the voltage or the current.

e. Channel B operates the same as channel A.

f. Turn off the power supply.

Note:

Not all power supplies have current limit/control capability and shorting the terminals like this on a piece of equipment that does **not** can destroy that piece of equipment due to large currents.

3.1.3 Digital Multimeter



figure 3. Fluke Multimeter (175)

3.1.3.1 Measure Resistance

4. Prepare the digital multimeter (DMM) to measure a resistance.

- a. Turn the large dial on the multimeter to select resistance measurement $\ \ensuremath{\Omega}$.
- b. Connect a red banana lead to the Ω input near the bottom of the device.
- c. Connect a black banana lead to the COM input of the device.
- d. When nothing is connected to the banana leads it should display 0L indicating an open circuit.
- e. When you short the red and black banana leads together it should display approximately 0.0 indicating a short circuit.

4-band Resistors

5. Use the multimeter to measure the 4-band resistors from RESISTORS A on the PC Board from the table below and record your measurements in the appropriate place on the results sheet.

RESISTORS A			
R1	R2	R3	R4
1.8k	4.7k	62k	4.7M

table 1. 4-band resistors

5-band Resistors

6. Use the multimeter to measure the 5-band resistors from RESISTORS B on the PC Board from the table below and record your measurements in the appropriate place on the results sheet.

RESISTORS B			
R5 R6 R7 R8			
1.00k	20.0k	40.2k	200k

table	2.	5-band	resistors
		0 00000	

Series Resistors

7. Place the following resistors in series and then use the multimeter to measure the total resistance across the resistors and record your measurements in the appropriate place on the results sheet.

Series Resistors				
RS1 RS2 RS3 RS4				
1.8k + 4.7k	4.99k + 40.2k	20.0k + 200k	5.6k + 10.0k + 20.0k	

table 3. resistors in series

Parallel Resistors

8. Place the following resistors in parallel and then use the multimeter to measure the total resistance across the resistors and record your measurements in the appropriate place on the results sheet.

Parallel Resistors			
RP1 RP2 RP3 RP4			
1.8k // 4.7k	4.99k // 40.2k	20.0k // 200k	5.6k // 10.0k // 20.0k

table 4. resistors in parallel

3.1.3.2 Measure DC Voltage

Note:

An ideal voltmeter is an open circuit.

- 9. Use the multimeter to measure a DC voltage.
 - a. Turn the large dial on the multimeter to select DC **Voltage** measurement ~V .
 - b. Connect a red banana lead to the V input and black banana lead to the COM input near the bottom of the multimeter.
 - c. When nothing is connected to the multimeter it should display 0.000 V DC.
 - d. Connect the other end of the red and black banana leads to the red + and black terminals of channel A of the power supply.
 - e. Turn on the power supply and verify that both independant and channel A are selected.
 - f. Use the voltage control knob for channel A to change the voltage and show that the voltage on the meter on the power supply is approximately the same as the display on the multimeter.
 - g. Use the needle display on the power supply to adjust the DC voltage to the following settings as close as possible; Then use the multimeter to record the corresponding measurements in the appropriate place on the results sheet.

Note:/ Make sure you are viewing the meter displays on the power supply directly from in front as viewing angle will effect measurement accuracy.

DC Voltage Measurements			
V1	V2	V3	
5V	10V	20V	

table 5. DC voltage measurements needle position

h. Turn off the power supply.

i. Disconnect the meter from the power supply.

3.1.3.3 Measure DC Current

Note:

An ideal ammeter is a short circuit.

- 10. Use the multimeter to measure a DC current.
 - a. Turn the large dial on the multimeter to select the **(mA)** measurement and press the yellow button to cycle between AC, DC and Hz. Cycle until you have the DC measurement selected.

Warning:

If you select the AC or Hz selection by mistake when trying to measure a DC quantity the meter will always read zero even if you apply a DC voltage.

b. Connect a red banana lead to the 400mA input and black banana lead to the COM input near the bottom of the multimeter.

Warning:

Do not exceed 400mA using these inputs as exceeding that current will blow the internal fuse. If a larger current measurement is desired connect the red banana lead to the 10A input at the buttom of the multimeter instead and use the corresponding large dial selection.

- c. When nothing is connected to the multimeter it should display ~ 0.00 mA DC.
- d. Connect the other end of the red and black banana leads to the red + and black terminals of channel A of the power supply.

Warning:

The power supply can output a maximum of 500mA when the current control knob is turned fully clockwise. As stated above the digital multimeter can only take a maximum of 400mA when on this input before the internal fuse will blow. Therefore, start with the current control knobs fully counter-clockwise and do not exceed the half way mark unless you are sure the output current is safely below 400mA.

e. Turn on the power supply and verify that both independant and channel A are selected.

- f. Use the current control knob for channel A to change the current and show that the current on the meter on the power supply is approximately the same as the display on the multimeter.
- g. Use the needle display on the power supply to adjust the DC current to the following settings as close as possible; Then use the multimeter to record the corresponding measurements in the appropriate place on the results sheet.

Note:

Make sure you are viewing the needle meter displays on the power supply directly from in front as viewing angle will effect measurement accuracy.

DC Current Measurements			
I1 I2 I3			
100mA	200mA	300mA	

table 6. DC current measurements needle position

h. Disconnect the meter from the power supply.

3.1.4 Power Supply Cont...

3.1.4.1 Series Mode

Series Mode

Puts the channel A supply in series with channel B supply for the purpose of doubling the available voltage.

11. Use the two channels A and B of the power supply in series mode.

a. Select the series mode using the series/parallel/independant switch on the power supply.

Note:

When series mode is selected the red terminal of channel B is internally connected to the black terminal of channel A so no external connection is required. Also when in this mode, only the channel A controls are used which controls both of channel A and B to the same value. Also note that the voltmeter on the power supply will only show either the channel A voltage or the channel B voltage but not the sum.

b. Setup the multimeter to measure the DC output voltage of the power supply as shown below.

Warning:

Remember to move the banana leads to the appropriate inputs of the multimeter and set the multimeter dial accordingly.



figure 4. DC Power Supplies Connected in Series)

c. Use the needle display on the power supply to adjust the DC voltage to the following settings as close as possible; Then use the multimeter to record the corresponding measurements in the appropriate place on the results sheet.

Power Supplies in Series		
V1	V2	V3

Power Supplies in Series				
V1 V2 V3				
5V	10V	20V		

table 7. series power supplies needle position

d. Turn off the power supply

3.1.4.2 Parallel Mode

Parallel Mode

Puts the channel A supply in parallel with channel B supply for the purpose of doubling the available current.

- 12. Use the two channels of the power supply in parallel mode.
 - a. Select the parallel mode using the series/parallel/independant switch on the power supply.

Note:

When parallel mode is selected the red terminals of channel A and B is internally connected, same with the black terminals, so no external connection is required. Also when in this mode, only the channel A controls are used which controls both of channel A and B to the same value. Also note that the ammeter on the power supply will only show either the channel A current or the channel B current but not the sum.

b. Setup the multimeter to measure the DC output current of the power supply as shown below. Use the 10A inputs on the multimeter and appropriate dial setting making sure to use the yellow button to enable the DC measurement.

Warning:

Use the 10A current inputs and settings on the multimeter as the current of the power supply can now significantly exceed the 400mA capability of the other input.



figure 5. DC Power Supplies Connected in Parallel)

c. Use the needle display on the power supply to adjust the DC current to the following settings as close as possible; Then use the multimeter to record the corresponding measurements in the appropriate place on the results sheet.

Power Supplies in Parallel				
A1 A2 A3				
100mA	200mA	400mA		

table 8. parallel power supplies - needle position

d. Remove the multimeter and place the power supply back into independent mode and turn it off.

3.1.5 Decade Box



figure 6. Ohmite Decade Box (Determ-ohm)

13. Measure the resistance of the decade resistance box using the multimeter at the following settings and record your measurements in the appropriate place on the results sheet.

Decade Box Resistances				
RD1 RD2 RD3 RD4				
1k	5k	12k	38k	

table 9. decade box settings

3.2 Ohms Law and Power Dissipation

Ohm's Law

The resistor's current I_R in amps (A) is equal to the resistor's voltage V_R in volts (V) divided by the resistance **R** in ohms (Ω):

$$I_{R} = \frac{V_{R}}{R} \quad \text{or} \quad V_{R} = I_{R} \cdot R \quad \text{or} \quad R = \frac{V_{R}}{I_{R}}$$
(1)
$$\left| \begin{array}{c} & & \\ &$$

Power Dissipated in Resistors

Any resistor in a circuit that has a voltage drop across it dissipates electrical power. This electrical power is converted into heat energy hence > all resistors have a power rating. This is the maximum power that can be dissipated from the resistor without it burning out. The rate of conversion is the power of dissipation.

$$P = I_R \cdot V_R \quad \text{or} \quad P = I_R^2 \cdot R \quad \text{or} \quad P = \frac{V_R^2}{R}$$
(2)

- 14. Use the Ohm's Law Test Circuit to compare a resistors stated value with the calculated value from Ohm's Law using its measured current and voltage at different operating points. The power dissipated by the resistor at each point can also be calculated. Complete the procedure for three different resistor values.
 - a. Connect the circuit in figure 1 using the following:
 - 1.8k resistor from the Student PC board.
 - The multimeter as a milliammeter.
 - Channel A as a voltage source from the DC power supply.
 - The appropriate banana leads.



figure 8. Ohm's Law Test Circuit

b. Use the multimeter to measure the current and the needle voltmeter display on the DC power supply to measure the voltage at each voltage setpoint below and record your result in the appropriate place on the results sheet.

Applied Voltages						
V1	V1 V2		V4	V5	V6	
20 V	10 V	5 V	-5 V	-10 V	-20 V	

table 10. six voltage testpoints

Note:

To apply a negative DC voltage across the resistor interchange the red and black banana plugs at the output terminals of the power supply.

- c. Replace the 1.8k resistor with a 4.7k resistor and make the same measurements again while recording your results in the appropriate place in the results sheet.
- d. Replace the resistor again with a 20.0k resistor and make the same measurements again while recording your results in the appropriate place in the results sheet.
- e. Turn off the power supply and disconnect the circuit.

3.3 Current Divider

Kirchoffs Current Law



figure 9. Kirchoffs Current Law

Kirchhoff's Current Law (KCL) is one of the fundamental laws used for circuit analysis. His current law states that for a parallel path the total current entering a circuits junction is exactly equal to the total current leaving the same junction. This is because it has no other place to go as no charge is lost.

In other words the algebraic sum of ALL the currents entering and leaving a junction must be equal to zero as: $\Sigma I_{IN} = \Sigma I_{OUT}$.

This idea by Kirchhoff is commonly known as the Conservation of Charge, as the current is conserved around the junction with no loss of current.

- 15. Use the Parallel Resistor Test Circuit to demonstrate that the supply current divides into both resistors according to Kirchoffs Current Law (KCL). You will be changing the value of one of the resistors to show how the change effects the circuit current flow and power dissipation.
 - a. Set the Decade Box to a resistance of $450 \Omega.$
 - b. Use the multimeter as a voltmeter to set channel A of the DC power supply to 15V. Turn the DC power supply **off** before proceeding to the next step.

c. Connect the circuit in figure 10 using the following:

- Use the DC power supply as a DC source.
- The multimeter as a milliammeter.
- 1.8k resistor from the Student PC Board for R₁.
- The Decade Box for R₂.
- The appropriate banana leads.



figure 10. Parallel Resistor Test Circuit

d. Turn the DC power supply back **on** and measure the supply current for each of the values of R₂ in the table below. Record each one in the appropriate place on the results sheet.

Decade Box Settings (Ω)							
R2_1	R2_2	R2_3	R2_4	R2_5	R2_6		
450	900	1.8k	3.6k	7.2k	14.4k		

table 11. R2 in parallel setpoints - decade box

Note:

Reducing the Decade Box Resistance below a certain value will cause the DC power supply to go into current control mode.

- e. Turn the DC power supply **off** and move the multimeter in the circuit so I_1 can now be measured.
- f. Turn the DC power supply back **on** and repeat the value's of R₂ with the milliammeter in its new position and record each reading in the appropriate place on the results sheet.
- g. Turn the DC power supply **off** and move the multimeter in the circuit so I_2 can now be measured.
- h. Turn the DC power supply back **on** and repeat the value's of R₂ with the milliammeter in its new position and record each reading in the appropriate place on the results sheet.
- i. Turn the DC power supply **off** and disconnect the circuit.

3.4 Voltage Divider

Kirchoffs Voltage Law



figure 11. Kirchoffs Voltage Law

Kirchhoff's Voltage Law (KVL) is the second of his fundamental laws we can use for circuit analysis. His voltage Law states that for a closed loop series path the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero. This is because a circuit loop is a closed conducting path so no energy is lost.

In other words the algebraic sum of ALL the potential differences around the loop must be equal to zero as: $\Sigma V = 0$. Note here that the term "algebraic sum" means to take into account the polarities and signs of the sources and voltage drops around the loop.

This idea by Kirchhoff is commonly known as the Conservation of Energy, as moving around a closed loop, or circuit, you will end up back to where you started in the circuit and therefore back to the same initial potential with no loss of voltage around the loop. Hence any voltage drops around the loop must be equal to any voltage sources met along the way.

- 16. For this test you will use the power supply to apply a voltage across two resistors in series while measuring both the current and the voltage across each of the resistors. This is to demonstrate that the voltage across the resistors divides according to Kirchoffs Voltage Law (KVL). You will be changing the value of one of the resistors to demonstrate how the voltage across the resistors changes.
 - a. Set the Decade Box to a resistance of 450Ω .
 - b. Use the multimeter as a voltmeter to set channel A of the DC power supply to 15V. Turn the DC power supply **off** before proceeding to the next step.

- c. Connect the circuit in figure 12 using the following:
 - Use the DC power supply as a DC source.
 - The multimeter as a milliammeter.
 - 1.8k resistor from the Student PC Board for R₁.
 - The Decade Box for R₂.
 - The appropriate banana leads.



figure 12. Series Resistor Test Circuit

d. Turn the DC power supply back **on** and measure the supply current for each of the values of R₂ in the table below. Record each one in the appropriate place on the results sheet.

Decade Box Settings (Ω)							
R2_1	R2_2	R2_3	R2_4	R2_5	R2_6		
450	900	1.8k	3.6k	7.2k	14.4k		

table 12.	R2 in	series	setpoints	-	decade	box
-----------	-------	--------	-----------	---	--------	-----

- e. Turn the DC power supply **off** and remove the multimeter from the circuit making sure to replace the milliammeter with a short circuit. Setup the multimeter as a DC voltmeter so the voltage across R₁ can now be measured.
- f. Turn the DC power supply back **on** and repeat the value's of R₂ with the multimeter in its new position and record each reading in the appropriate place on the results sheet.
- g. Turn the DC power supply **off** and move the multimeter in the circuit so the voltage across R₂ can now be measured.
- h. Turn the DC power supply back **on** and repeat the value's of R₂ with the multimeter in its new position and record each reading in the appropriate place on the results sheet.
- i. Turn the DC power supply **off** and disconnect the circuit.

3.5 Loading Effect

Non-ideal Voltmeter



figure 13. Non-ideal Voltmeter

An ideal voltmeter imposes no load on the circuit being measured so as to not disturb the circuit. In practice, voltmeters draw some current and hence some small amount of load to the circuit affecting results.

So in an ideal voltmeter, the resistance of the meter is infinite.

In practice, voltmeters originally had resistance of several thousand ohms, $30K\Omega$ or $100K\Omega$ was common. The resulting power used was required to deflect a moving needle galvanometer type meter.

Later electronic meters with input amplifiers such as your Vacuum tube and transistorized volt meters drew much less current with very high impedance and active amplifiers to drive the meter movements; today's digital multimeters are typically set at 10,000,000 Ω .



little voltage to be dropped as possible while conducting current.

- 17. Use the Non-ideal Voltmeter Test Circuit to demonstrate that a practical voltmeter can give you large errors in your measurements if you are not careful due to the loading effect.
 - a. Use the multimeter as a voltmeter to set channel A of the DC power supply to 11.5V. Turn the DC power supply **off** before proceeding to the next step.
 - b. Connect the Circuit in the figure below using the following.
 - Use the DC power supply as a DC source.
 - The multimeter as a voltmeter.
 - The 4.7M and 6.8M resistors from the Student PC Board for R₁ and R₂ respectively.
 - The appropriate banana leads



figure 15. Non-ideal Voltmeter Test Circuit

- c. Turn the DC power supply back **on** and using the multimeter first measure the voltage across R_1 and then move the multimeter to then measure the voltage across R_2 and record both in the appropriate place on the results sheet.
- d. Turn the DC power supply **off** and disconnect the circuit.

3.6 Clean-up

18. Cleanup your station, everything should be returned to where you got it from. Verify your results with an instructor or TA to show that you have completed everything and once everything is completed and tidy get a signature on your Results page before you leave.

4 Post-Lab

The following is what you are expected to hand-in one week (by 4:00pm) after completion of the lab. You only have to handin one copy per group. There is an assignment box in the D-ICE pedway located just before the elevators marked ECE202 Lab. Please staple everything together in the following order:

- Use the first page of your **Result Sheet** as your cover page. Make sure your names, student IDs, CCID's and lab section are clearly writen in the table at the top of the page. Your results sheet should be signed twice by the laboratory instuctor or teaching assistant, once at the beginning of the lab to show that you have completed your prelab and once when you have completed the lab and finished cleaning up.
- The remaining completed **Results Sheets** in order with all calculations, results and graphs as required.
- The completed **Post-lab Questions** below on a separate piece of paper.

4.1 Calculations

Complete the tables on your Results sheet by completing the following calculations. Everything in light red on the results sheet is part of the postlab calculations.



- 1. For the RESISTORS A and B calculate the percent error of your resistor measurements.
- 2. For the Power Supply as a Voltage Source and Current Source calculate the difference error between your needle reading and your multimeter measurement.
- 3. For the Ohm's Law and Power Dissipation calculate the resistance by using ohms law and the power by using the power equation.

- 4. For the Current Divider calculate the input power (P_S), the power dissipated by each resistor (P_{R1} and P_{R2}) and the total dissipated power ($P_{R1} + P_{R2}$).
- 5. For the Voltage Divider calculate the input power (P_S), the power dissipated by each resistor (P_{R1} and P_{R2}) and the total dissipated power ($P_{R1} + P_{R2}$).
- 6. For the Loading Effect calculate the percent error for your voltage measurements.

4.2 Graphs

Using the provided graphs in your results sheet make the following plots:

- 1. **Resistor I-V Curves** Using the result from Ohms Law and Power create 3 separate plots showing each resistors ($R_{1.8k}$, $R_{4.7k}$ and $R_{20.0k}$) current vs. voltage.
- 2. **Resistor P-V Curves** Using the result from Ohms Law and Power create 3 separate plots showing each resistors (R_{1.8k}, R_{4.7k} and R_{20.0k}) power vs. voltage.
- 3. **Current Divider Current** Using the results from the Current Divider create 3 separate plots showing each branch current (I_s, I₁ and I₂) vs. the resistance setting of R₂.
- 4. **Current Divider Power** Using the results from the Current Divider create 3 separate plots showing each power $(P_{R1}+P_{R2}, P_{R1} \text{ and } P_{R2})$ vs. the resistance setting of R_2 .
- 5. **Voltage Divider Voltage** Using the results from the Voltage Divider create 3 separate plots showing each voltage $(V_s, V_1 \text{ and } V_2)$ vs. the resistance setting of R_2 .
- 6. **Voltage Divider Power** Using the results from the Voltage Divider create 3 separate plots showing each power $(P_{R1}+P_{R2}, P_{R1} \text{ and } P_{R2})$ vs. the resistance setting of R_2 .

4.3 Questions

Answer the following questions on a separate piece of paper to hand in with your Results Sheet. Make sure to include an appropriate title, your first and last name, CCID, student ID and your lab section at the top of the page.

- 1. For the resistance measurements you took using your multimeter on both the 4-band and 5-band resistors do they fall within the tolerance boundries of the each Resistor? If not, explain.
- 2. Looking at the Resistor I-V Curves graph what does the slope of the each curve represent? Does each Resistor you plotted show a constant slope? If a Resistor doesn't show a constant slope what does that mean? What does it mean if a resistor has a steep or a shallow slope? What does it mean if a resistor has a completely vertical or horizontal slope?
- 3. Looking at the Resistor P-V Curves graph the power is always positive. Explain in your own words what this means? What happens to the Power dissipated in the resistor when you double the voltage? Explain.
- 4. Using a 1/4 watt resistor across the terminals of channel A of the DC power supply what is the maximum resistance that can be used without exceeding its ratings and still be able to obtain the power supplies maximum current? Show your work.
- 5. Again using a 1/4 watt resistor across the terminals of channel A of the DC power supply what is the minimum resistance that can be used without exceeding its ratings and still be able to obtain the power supplies maximum voltage? Show your work.
- 6. What would the rating for power and resistance of a resistor placed across the terminals of channel A of the power supply be while you tried to draw maximum power? Show your work.
- 7. Looking at the results and graphs from the Current Divider do they support KCL (Kirchoffs Current Law)? Use your results to explain.
- 8. Looking at the results and graphs from the Voltage Divider do they support KVL (Kirchoffs Voltage Law)? Use your results to explain.
- 9. Using your measured results for V_{S} , V_1 and V_2 from The Loading Effect calculate what the internal resistance of the non-ideal voltmeter is for both cases: the first is when you measured V_1 and the second is when you measured V_2 . Show your work.