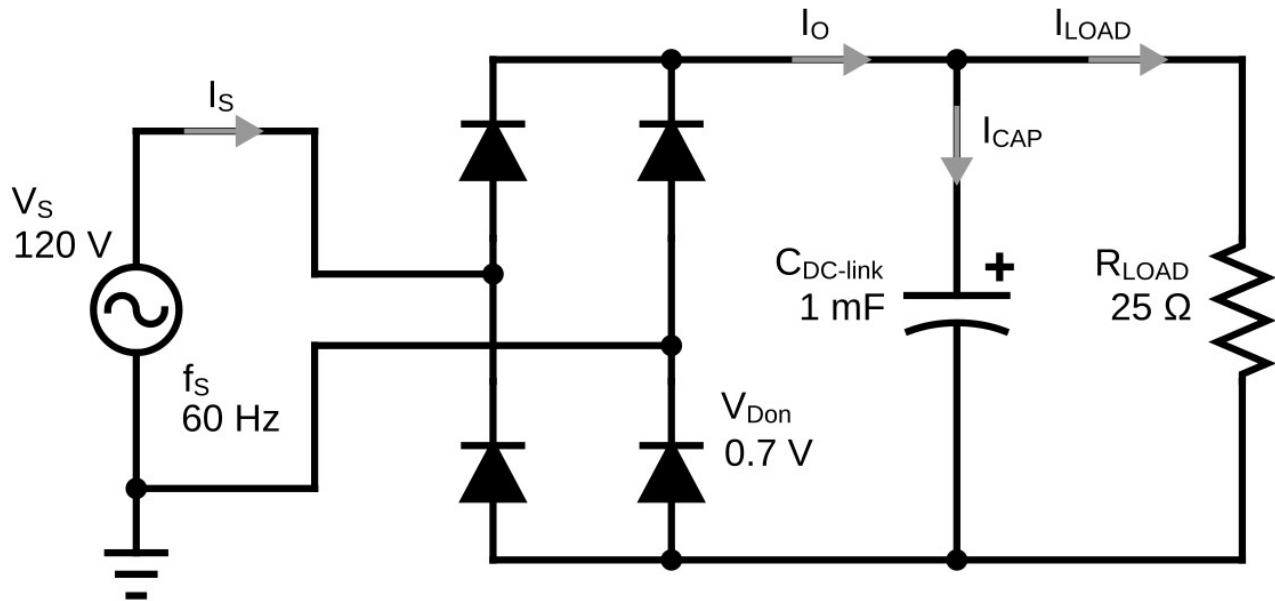


Prelab 1: Calculations Worksheet

ECE 401 – Power Electronics



Parameters: $V_S = 120\text{ V}$, $f_S = 60\text{ Hz}$, $C = 1\text{ mF}$, $R_{LOAD} = 25\text{ }\Omega$, $V_{Don} = 0.7\text{ V}$

- i. Use the included iteration method template to calculate θ_C , V_R , V_{DC} and I_{DC} .
(Show your work in the space provided).

Step 1: Use these equations to calculate starting values for V_R , V_{DC} and I_{DC} . assume: $\theta_C \approx 0$.

Assume: $\theta_C \approx 0$ I_{DC} not known $V_{PK} \approx V_{DC}$		$V_m = \sqrt{2} V_s$ $V_{DC} \approx V_m - 2V_{Don}$ $V_{DC} \approx$	$I_{DC} = \frac{V_{DC}}{R_{LOAD}}$ $I_{DC} =$
	$V_R = \frac{I_{DC}}{2f_s C}$ $V_R =$	$V_{DC} = V_{PK} - \frac{V_R}{2}$ $V_{DC} =$	$I_{DC} = \frac{V_{DC}}{R_{LOAD}}$ $I_{DC} =$

Step 2: Use these equations for an iteration approach to obtain values for θ_C , V_R , V_{DC} and I_{DC}

$\theta_C = 2 \times \cos^{-1} \left(1 - \frac{V_R}{V_m} \right)$	$V_R = \frac{I_{DC}}{2f_s C} \left(1 - \frac{\theta_C}{\pi} \right)$	$V_{DC} = V_{PK} - \frac{V_R}{2}$	$I_{DC} = \frac{V_{DC}}{R}$
1 st Iteration			
2 nd Iteration			
3 rd Iteration			
4 th Iteration			

ii. Calculate the rms and peak of the output and capacitor currents (I_m , $I_{O,rms}$, I_C , $I_{C,pk}$).

(Show your work in the space provided).

$I_m = \frac{\pi^2}{2\theta_C} I_{DC}$	$I_m =$
$I_{O,rms} = I_S = I_{DC} \sqrt{\frac{\pi^3}{8\theta_C}}$	$I_{O,rms} =$
$I_C = I_{DC} \sqrt{\frac{\pi^3}{8\theta_C} - 1}$	$I_C =$
$I_{C,pk} = I_m - I_{DC}$	$I_{C,pk} =$

iii. Calculate diode rectifier input power factor (PF).

(Show your work in the space provided).

$P_S = P_{LOAD} + 2I_{DC} V_{Don}$	$P_S =$
$S_S = I_S V_S$	$S_S =$
$PF = \frac{P_S}{S_S}$	$PF =$

iv. Calculate the following remaining parameters.
(Show your work in the space provided).

$V_{O,RMS} =$		$P_{LOAD} =$	
$V_{O,AC} =$		$S =$	
$V_{R,RMS} =$		$P_S =$	
$I_{O,RMS} =$		$P_F =$	
$I_S =$		$I_{LOAD,DC} =$	
$I_{O,AC} =$		$I_{LOAD,AC} =$	
$I_{C,RMS} =$			